



Chapter 09

Network Theorems

Contraction Contractico Contra







Algebraically combine results









Find I_L $E_{20 V}$ I_L R_1 I_L R_1 I_L R_L R_L R_L



6











Thévenin's Theorem Any linear bilateral network can be reduced to a simplified two-terminal circuit with a single voltage source in series with a single resistor Voltage source: Thévenin equivalent voltage, E_{Th}. Series resistance: Thévenin equivalent resistance, **R**_{Th}. R_{Th} R_1 I. $\circ a$ 1 $6 k\Omega$ R_L 0 \rightarrow 5 k Ω R_L 0 \rightarrow 5 k Ω E_{Th} Ε 15 V I (1) 5 mA R_2 $\sum 2 k\Omega$ I h 10 C-C Tsai

Thévenin's Theorem

Steps to convert to a Thévenin circuit

- Identify and remove load from circuit
- Replace voltage sources with shorts, current sources with opens to determine Thévenin equivalent resistance as seen by open circuit.
- Replace sources and calculate voltage across open (<u>If there is more than one source,</u> <u>Superposition theorem could be used</u>) to **determine Thévenin equivalent voltage** as seen by open circuit.
- Draw Thévenin equivalent circuit, including load

11

C-C Tsai















Steps to convert to a Norton circuit

- Identify and remove load from circuit
- Determine open-circuit resistance, i.e., Norton equivalent resistance.
- Replace sources and determine current that would flow through a short place between two terminals. This current is the Norton equivalent current
- For multiple sources, superposition theorem could be used
- Draw the Norton equivalent circuit including the load



Norton's Theorem

 Norton equivalent circuit may be determined directly from a Thévenin circuit by using source transformation theorem







Maximum Power Transfer

- A load resistor will receive maximum power from a circuit when its resistance is the same as the Thévenin (or Norton) equivalent resistance
- Calculate maximum power delivered by source to load by using $P = V^2/R$
- Voltage across load is <u>one half of Thévenin</u> <u>equivalent voltage</u>
- Current through load is one half of Norton equivalent current













Efficiency

 Calculate the efficiency of maximum power transfer

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%$$

$$\eta = \frac{\frac{E_{\text{Th}}^2}{4R_{\text{Th}}}}{\frac{E_{\text{Th}}^2}{2R_{\text{Th}}}} \times 100\% = 50\%$$











Using Millman's theory







 Find both the Thévenin and the Norton equivalent circuits external to the load resistor in the circuit shown

















- **1.** Can use Superposition Theory for solving the unknown voltage and current of a circuit.
- 2. Can apply Thévenin's Theory for solving the unknown voltage and current of a circuit.
- 3. Can apply Norton's Theory for solving the unknown voltage and current of a circuit.
- 4. Can use Maximum Power Transfer for solving the output power.
- 5. Can recognize Millman's Theory for solving unknown voltage and current of a circuit.

C-C Tsai