

Chapter 11


Capacitors Charging, Discharging, Simple Waveshaping Circuits

 Source: Circuit Analysis: Theory and Practice ©Delmar Cengage Learning



Introduction

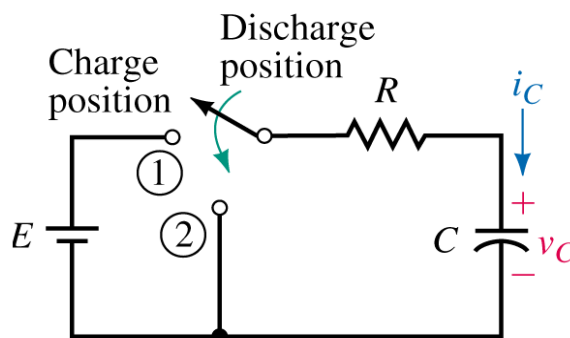- When switch is closed at ①, **capacitor charging**
- When switch is closed at ②, **capacitor discharging**
- **Transient voltages and currents** result when circuit is switched




 C-C Tsai

2

Capacitor Charging

When switch is closed at ①, beginning state

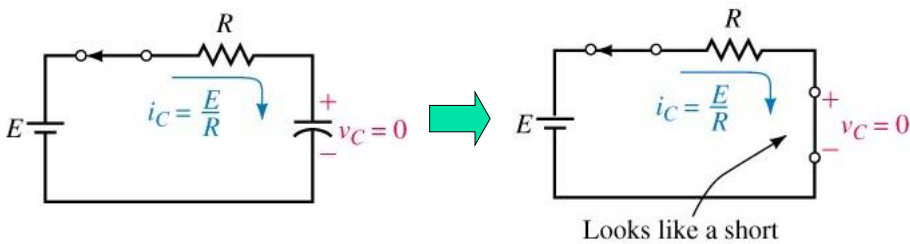- Capacitor voltage cannot change instantaneously
- When switching, the capacitor looks like a short circuit
- **Capacitor voltage** begins at **zero**
- **Capacitor current** instantaneously jumps to E/R




C-C Tsai

3

Capacitor Charging

When switch is closed at ①, transient state

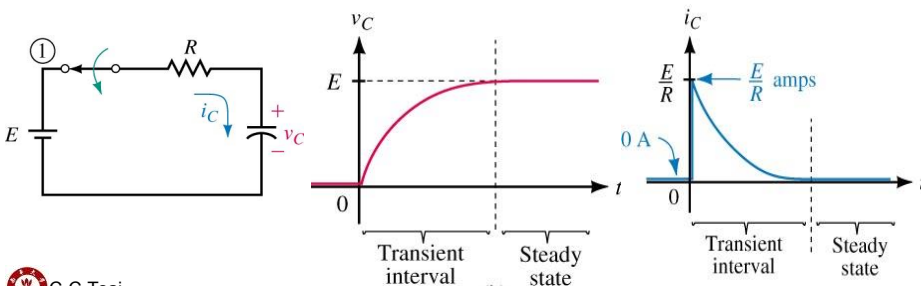
- **Capacitor voltage** begins at zero and exponentially increases to E volts
- **Capacitor current** instantaneously jumps to E/R and exponentially decays to zero



C-C Tsai

4

Capacitor Charging Process

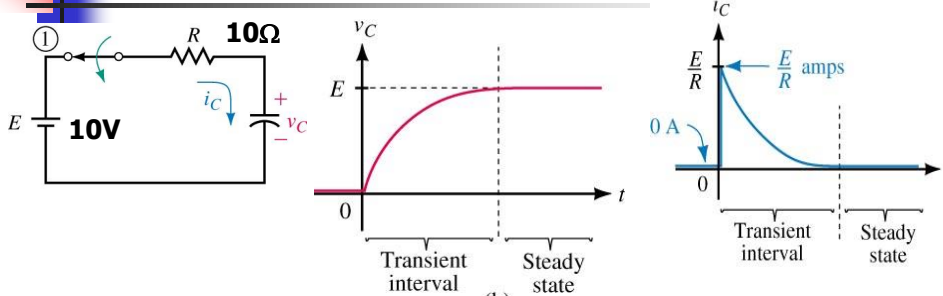

$$t=0s, v_C = 0V, i_C = (E - v_C)/10 = (10 - 0)/10 = 1A$$

$$t=1s, v_C = 6.3V, i_C = (E - v_C)/10 = (10 - 6.3)/10 = 0.37A$$

$$t=3s, v_C = 9.5V, i_C = (E - v_C)/10 = (10 - 9.5)/10 = 0.05A$$


$$t=5s, v_C = 10V, i_C = (E - v_C)/10 = (10 - 10)/10 = 0A$$

$$t=6s, v_C = 10V, i_C = (E - v_C)/10 = (10 - 10)/10 = 0A$$

Steady State Conditions

When switch is closed at ①, **steady state**

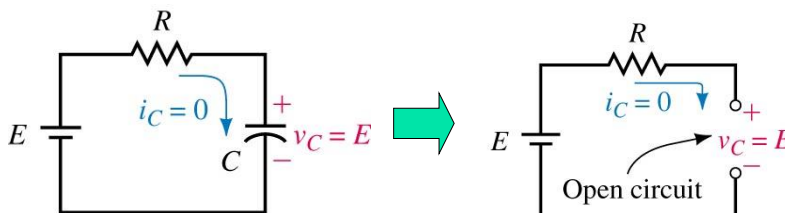
- Capacitor voltage and current reach their final values and **stop changing**
- Capacitor has voltage across it, but no current flows through the circuit. **Capacitor looks like an open circuit.**




Capacitor Discharging

When switch is closed at ②, beginning state

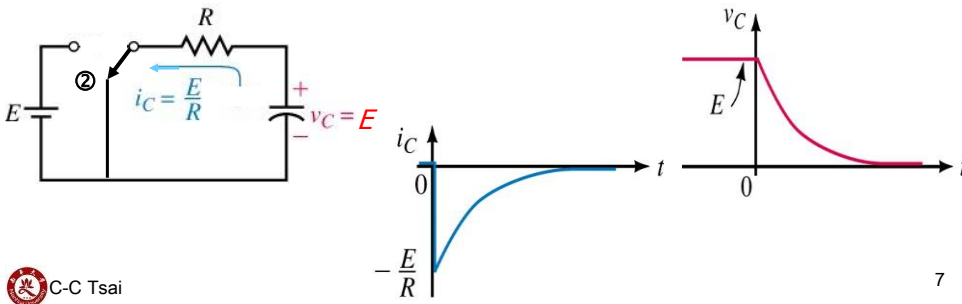- **Capacitor voltage** has E volts across it when it begins to discharge
- **Capacitor current** will instantly jump to $-E/R$
- Both voltage and current will **decay exponentially to zero**




Capacitor Discharging Process

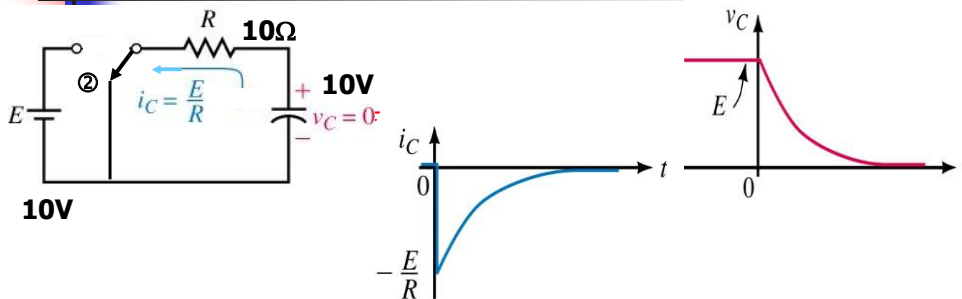


- $t=0s, v_c = 10V, i_c = -(v_c)/10 = -(10)/10 = -1A$
 $t=1s, v_c = 3.7V, i_c = -(v_c)/10 = -(3.3)/10 = -0.37A$
 $t=3s, v_c = 0.5V, i_c = -(v_c)/10 = -(0.5)/10 = -0.05A$
 $t=5s, v_c = 0V, i_c = -(v_c)/10 = (0)/10 = 0A$
 $t=6s, v_c = 0V, i_c = -(v_c)/10 = (0)/10 = 0A$

Example: Capacitor Charging/Discharge

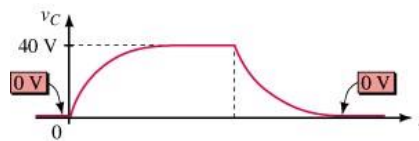

(a)

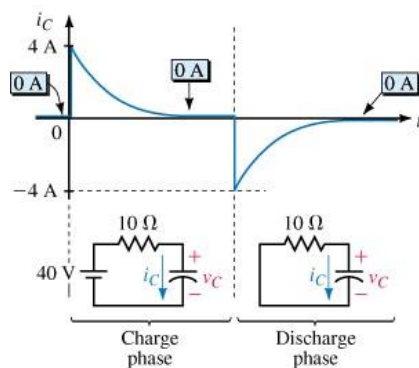

Capacitor Charging Equations





- Voltages and currents in a charging circuit do not change instantaneously
- These changes over time are **exponential** changes
- **The voltage** across the capacitor as a function of time is

$$v_C = E(1 - e^{-t/RC})$$

- **The current** through the capacitor as a function of time is

$$i_C = \frac{E}{R} e^{-t/RC}$$

Capacitor Charging Equations

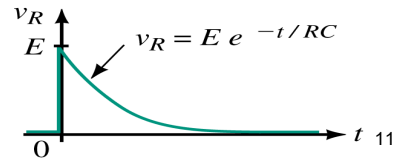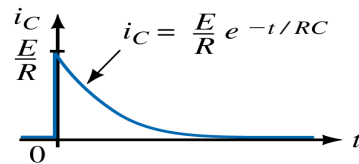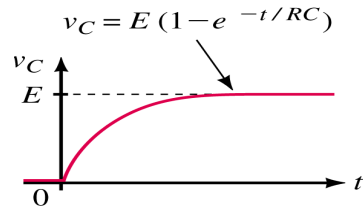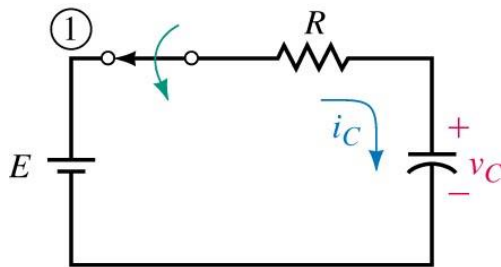

 C-C Tsai

The Time Constant

- Rate at which a capacitor charges **depends on product of R and C**
- Product known as **time constant, $\tau = RC$**
 τ (Greek letter tau) has units of seconds
- Length of time that a transient lasts depends on **exponential function $e^{-t/\tau}$** .
- As t increases, the function decreases. When the t reaches infinity, the function decays to zero
- For all practical purposes, **transients can be considered to last for only five time constants**

 C-C Tsai

12

Exponential Functions

x	e^{-x}	$1 - e^{-x}$
0	1	0
1	0.3679	0.6321
2	0.1353	0.8647
3	0.0498	0.9502
4	0.0183	0.9817
5	0.0067	0.9933

The Time Constant

The functions $e^{-t/\tau}$ and $1 - e^{-t/\tau}$

$$v_C = E(1 - e^{-t/RC})$$

$t = 0RC = 0\tau$, $e^{-0} = 1$, $E(1 - e^{-0}) = 0$


$t = 1RC = 1\tau$, $e^{-1} = 0.368$, $E(1 - e^{-1}) = 0.632 \times E$

$t = 2RC = 2\tau$, $e^{-2} = 0.135$, $E(1 - e^{-2}) = 0.865 \times E$


$t = 3RC = 3\tau$, $e^{-3} = 0.050$, $E(1 - e^{-3}) = 0.950 \times E$

$t = 4RC = 4\tau$, $e^{-4} = 0.018$, $E(1 - e^{-4}) = 0.982 \times E$

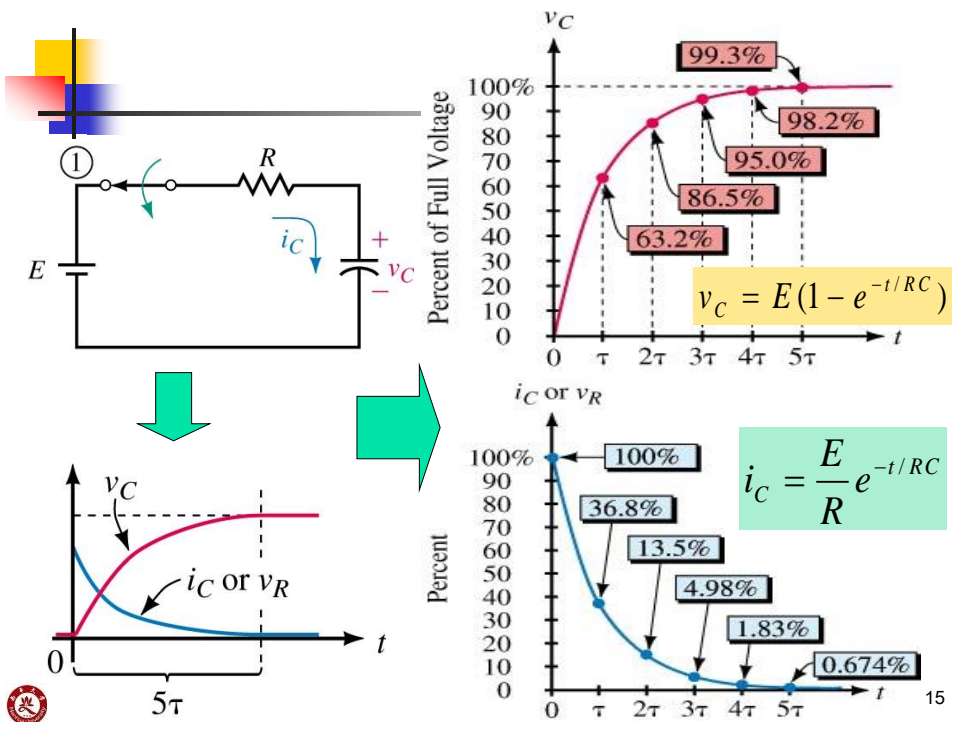$t \geq 5RC = 5\tau$, $e^{-5} = 0.007$, $E(1 - e^{-5}) = 0.993 \times E$






The Time Constant

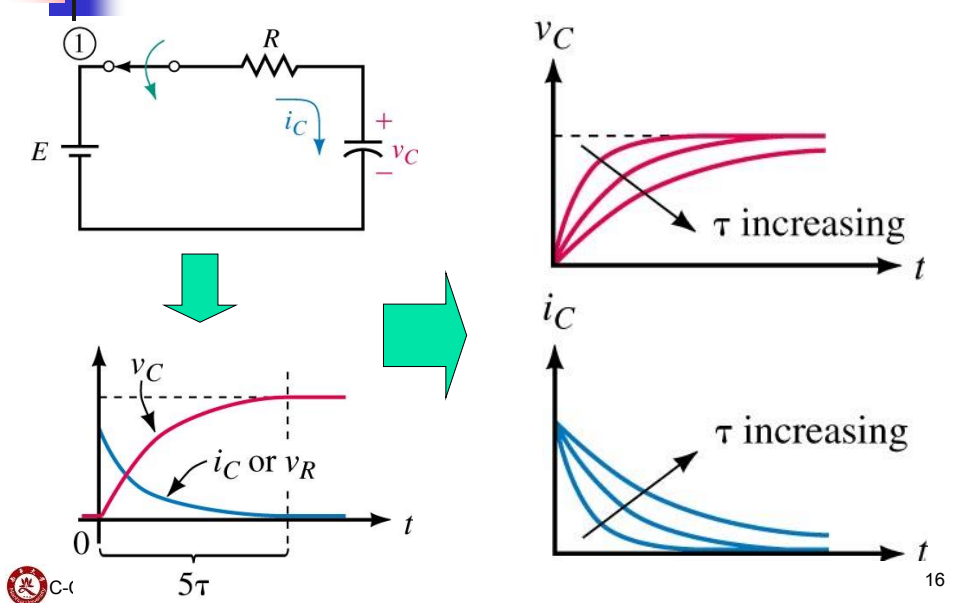


Example1: Capacitor Charging

A RC circuit with $E=100\text{V}$, $R=10\text{K}\Omega$, and $C=10\mu\text{F}$

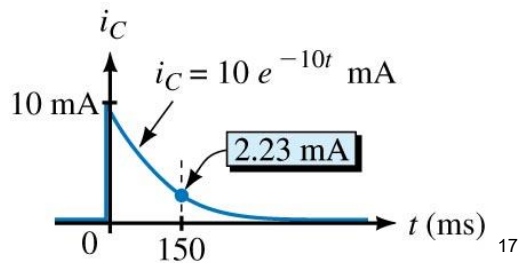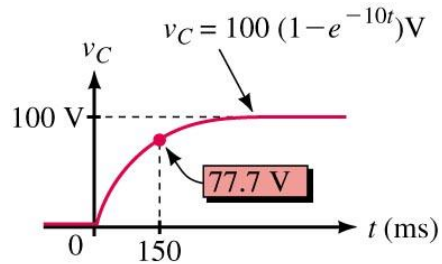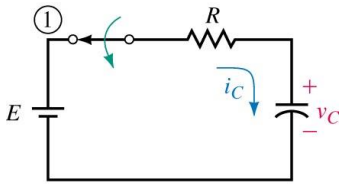


Example2: Capacitor Charging

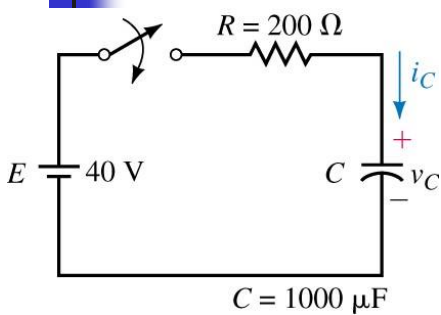

Capacitor with an Initial Voltage



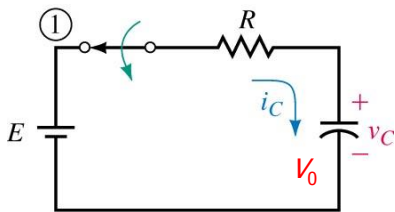
- Voltage denoted as V_0
 - Capacitor has a voltage on it
- Voltage and current in a circuit will be affected by initial voltage



$$v_C = E + (V_0 - E)e^{-t/\tau}$$


$$i_C = \frac{E - V_0}{R}e^{-t/\tau}$$

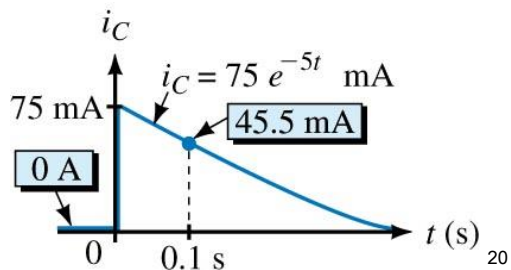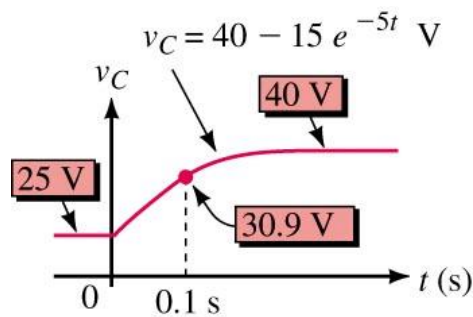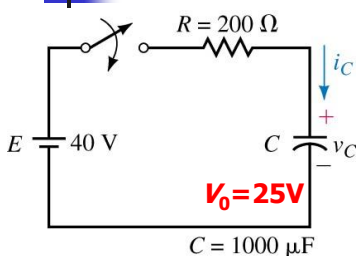Example: Capacitor with an Initial Voltage



Capacitor Discharging Equations

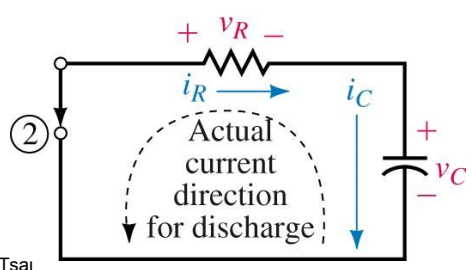- If a capacitor is **charged to voltage V_0** and **then discharged**.
- Current is negative because it flows opposite to reference direction
- Discharge transients last five time constants
- All voltages and currents are at zero when capacitor has fully discharged



$$v_C = V_0 e^{-t/\tau}$$




$$v_R = -V_0 e^{-t/\tau}$$

$$i_C = -\frac{V_0}{R} e^{-t/\tau}$$

C-C Tsai

21

Capacitor Discharge Equations

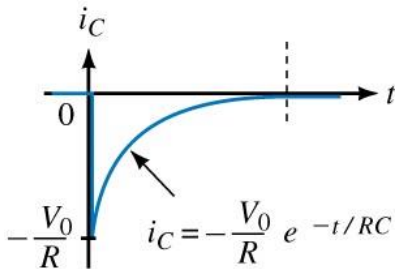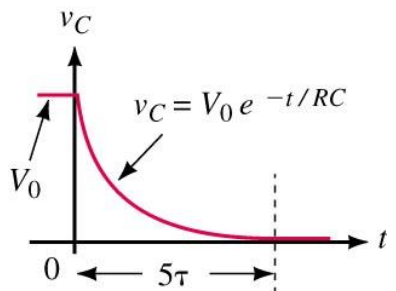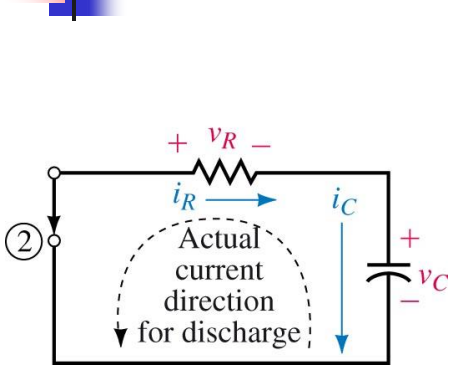


C-C Tsai

22

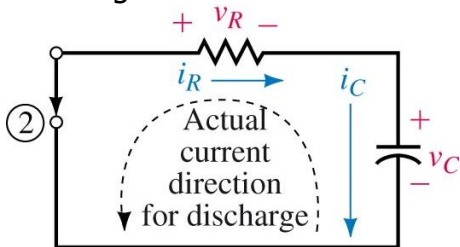
Example: Capacitor Discharge

A RC circuit with $R=5\text{K}\Omega$ and $C=25\mu\text{F}$, assume that C has charged to 100V . Determine the discharge voltage and current.




More Complex Circuits

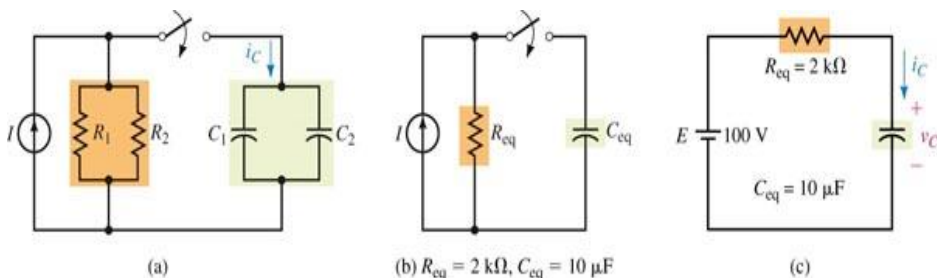
- Remove capacitor as the load and determine **Thévenin equivalent circuit**
- Use R_{Th} to determine τ , $\tau = R_{\text{Th}} \cdot C$
- Use E_{Th} as the equivalent source voltage



Example: More Complex Circuits


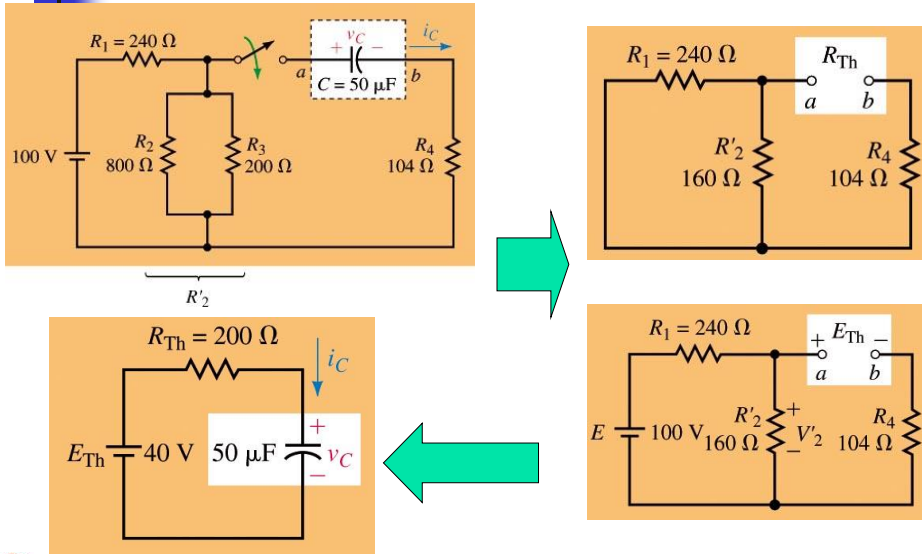


Example: More Complex Circuits

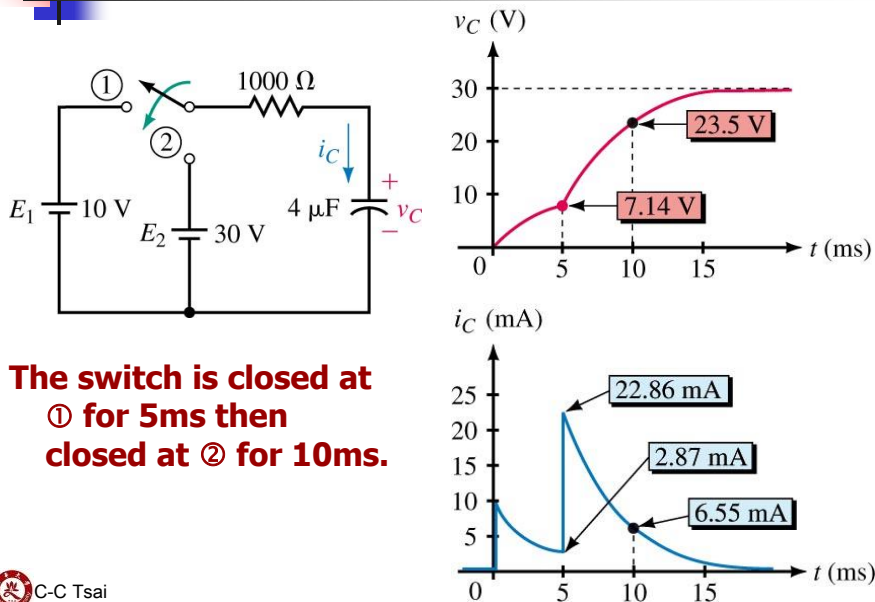

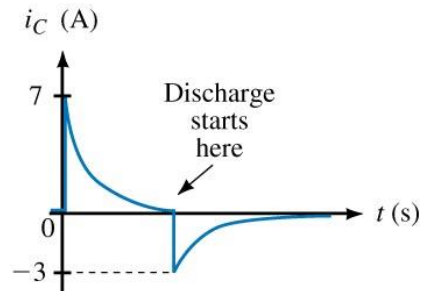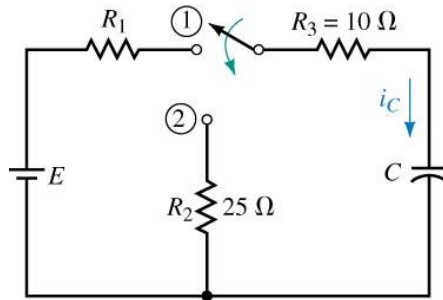
Example: More Complex Circuits

The capacitor takes **1.75ms** to discharge as shown the waveform. Determine E , R_1 , and C .




An RC Timing Applications

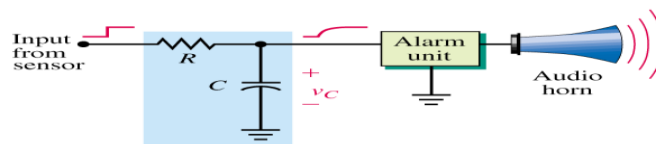- RC circuits are used to **create delays for alarm, motor control, and timing applications**
- Alarm unit shown contains a threshold detector**
 - When input to this detector exceeds a preset value, the alarm is turned on




(a) Delay circuit

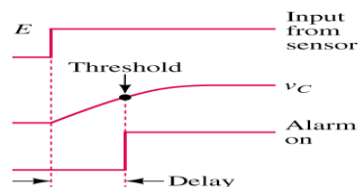

Pulse Response of RC Circuits

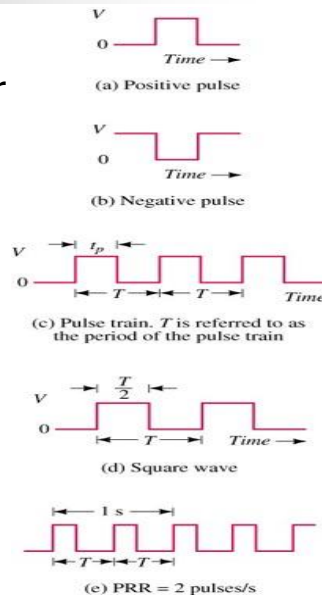
- **Pulse:** Voltage or current that changes from one level to another and back again
- **Periodic waveform:** Pulse train is a repetitive stream of pulses
- **Square wave:** Waveform's time high equals its time low
- **Frequency:** Number of pulses per second
- **Duty cycle:** Width of pulse compared to its period



 C-C Tsai

Pulse Response of RC Circuits

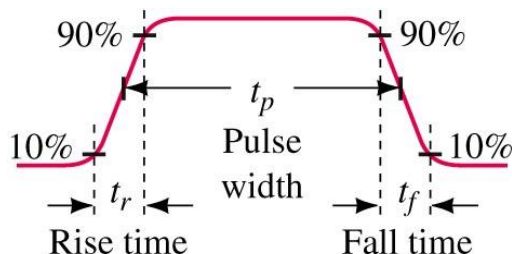- Pulses have a rise and fall time
 - Because they do not rise and fall instantaneously
- **Rise and fall times** are measured between the 10% and 90% points





 C-C Tsai

30

The Effect of Pulse Width

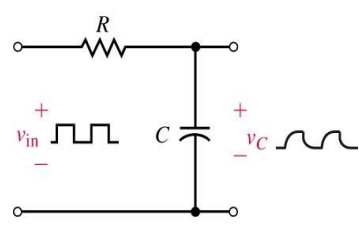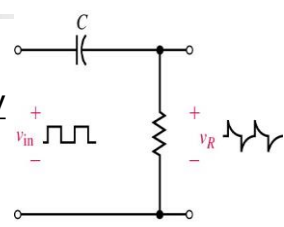- If pulse width $t_p \gg 5\tau$
 - Capacitor charges and discharges fully
 - This is a **differentiator circuit**
- If pulse width $t_p = 5\tau$
 - Capacitor fully charges and discharges during each pulse
- If the pulse width $t_p \ll 5\tau$
 - Capacitor **cannot** fully charge and discharge
 - This is an **integrator circuit**





C-C Tsai




31

Simple Waveshaping Circuits

$T \gg 5\tau$

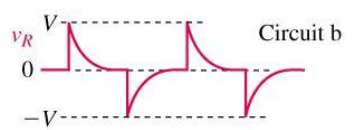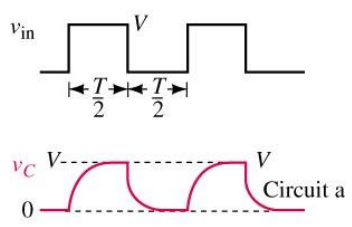

$T \ll 5\tau$

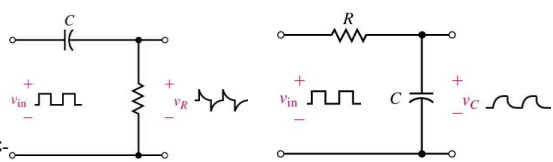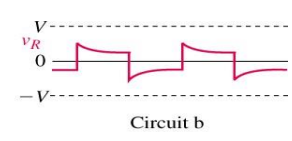
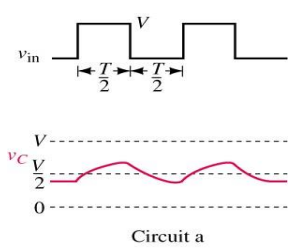


C-C

32



Simple Waveshaping Circuits

$$T \ll 5\tau$$

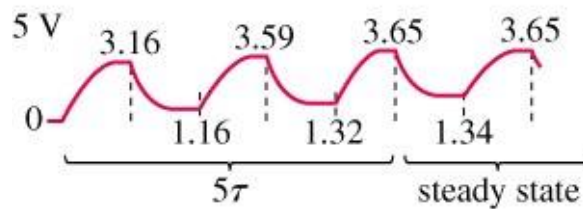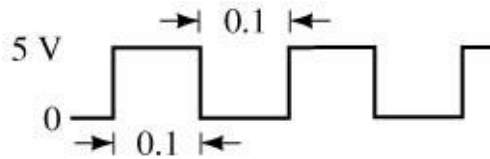


Capacitive Loading

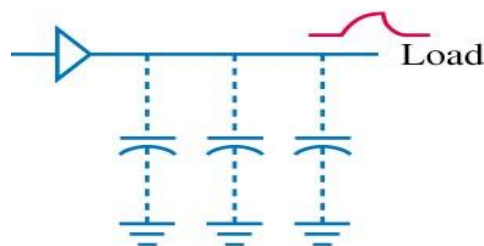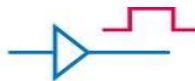- In high-speed circuits, the capacitance can cause problems




Transient Analysis Using Computers

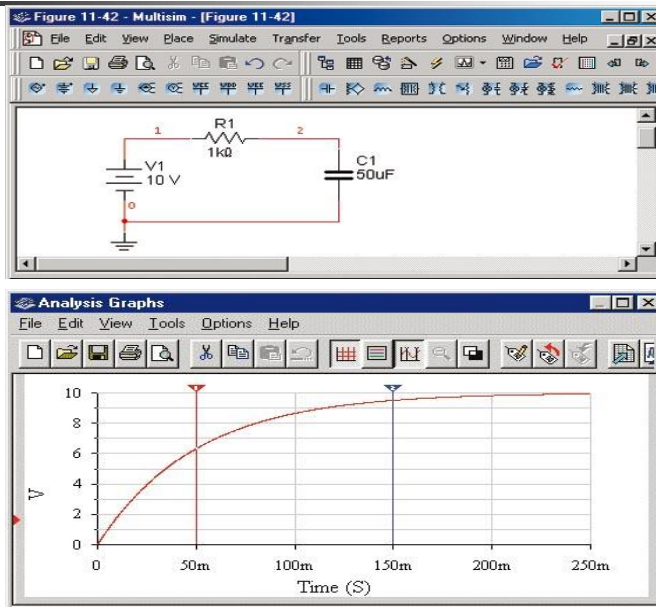


C-C Tsai

35

Transient Analysis Using Multisim

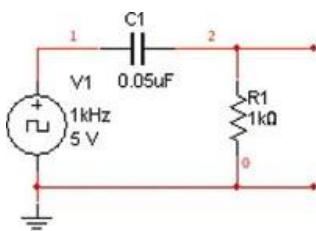

(a)

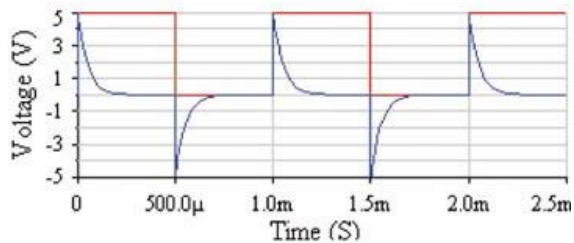


(b) The red waveform is the input and the blue one is the output

C-C Tsai


36

Problem: Draw the V_C waveform

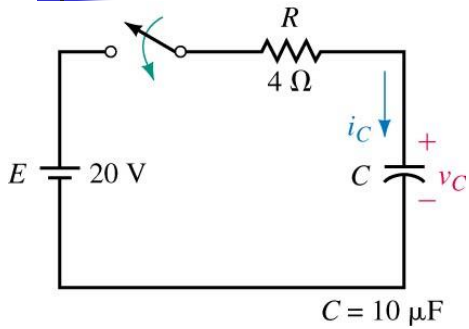

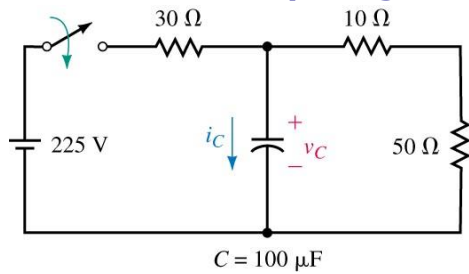Problem:


Draw the V_C waveform after closing the switch for 15ms and opening the switch.





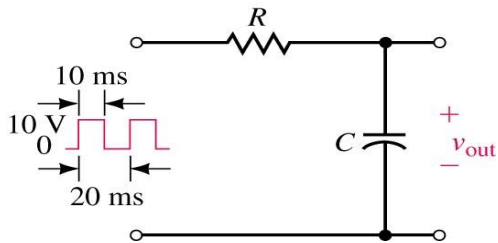Problem:

Draw the V_{out} waveform if (a) $R=2K\Omega$ and $C=0.1\mu F$ and (b) $R=20K\Omega$ and $C=1\mu F$.



Problem:

If $V_C = 4.75V$ the alarm will be on, how long is required when the switch is closed to 5V.

