

Chapter 14

Inductive Transients



Source: Circuit Analysis: Theory and Practice ©Delmar Cengage Learning



Transients

- Voltages and currents during a transitional interval
 - Referred to as transient behavior of the circuit
- **Capacitive circuit**
 - Voltages and currents undergo transitional phase
 - **Capacitor charges and discharges**
- **Inductive circuit**
 - Transitional phase occurs as the magnetic field builds and collapses



C-C Tsai

2



Voltage Across an Inductor

- Induced voltage across an inductor is proportional to rate of change of current



$$v_L = L \frac{\Delta i}{\Delta t}$$

- If inductor current could change instantaneously
 - Its rate of change would be infinite
 - Would cause infinite voltage
- Infinite voltage is not possible
 - Inductor current cannot change instantaneously**
 - It cannot jump from one value to another**, but must be **continuous at all times**

Transient due to Inductor

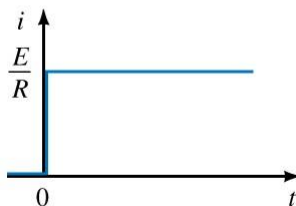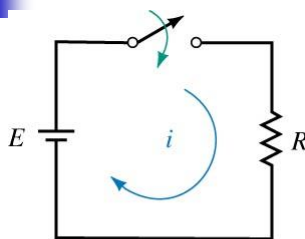

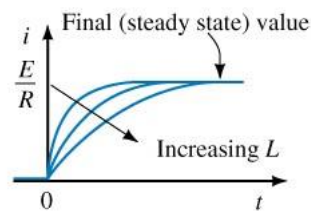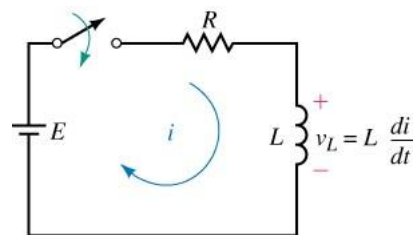
(a) No transient occurs in a purely resistive circuit.



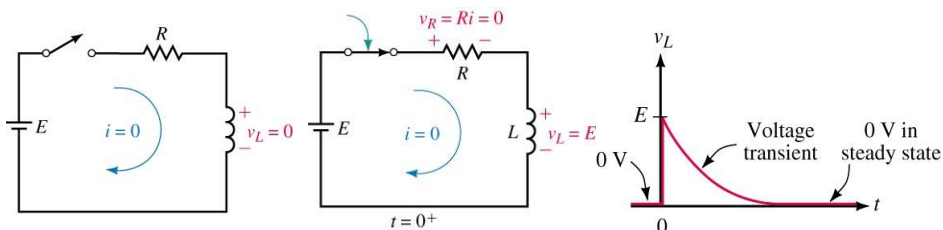(b) Adding inductance causes a transient to appear. R is held constant here.

Inductor Voltage

- Immediately after closing the switch on an RL circuit
 - Current is zero
 - Voltage across the resistor is zero
- Voltage across resistor is zero
 - Voltage across inductor is source voltage
- Inductor voltage will then exponentially decay to zero




C-C Tsai

5

Open-Circuit Equivalent

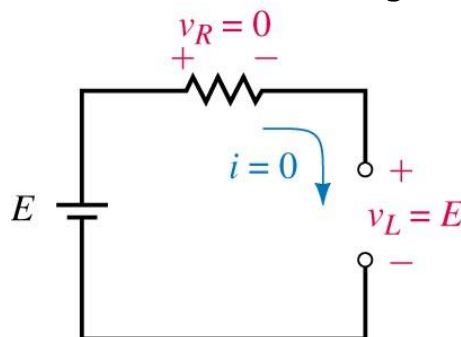- After switch is closed ($t=0^+$)
 - Inductor has voltage across it and no current through it
- Inductor with zero initial current looks like an open circuit at instant of switching




C-C Tsai

6

Initial Condition Circuits

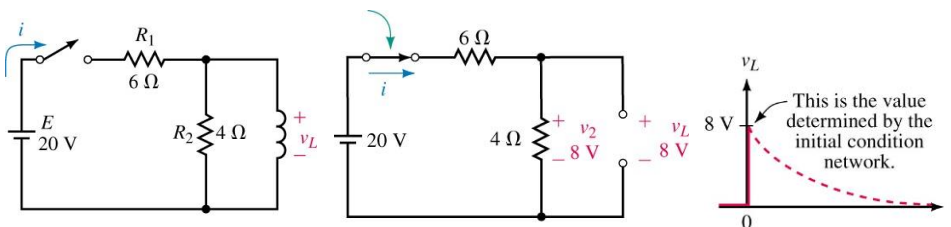- Voltages and currents in circuits immediately after switching ($t=0^+$)
 - Determined from the open-circuit equivalent
- **By replacing inductors with opens**
 - We get initial condition circuit
- Initial condition networks
 - Yield voltages and currents only at switching




C-C Tsai

7

Circuit Current and Circuit Voltages

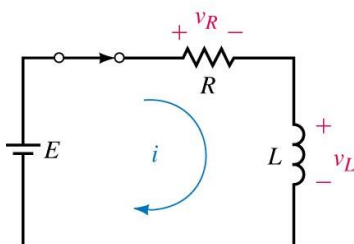- **Current $i(t)$** in an RL circuit is an exponentially increasing function of time
- Current begins at zero and rises to a maximum value
- **Voltage across resistor V_R** is an exponentially increasing function of time
- **Voltage across inductor V_L** is an exponentially decreasing function of time



$$i(t) = \frac{E}{R} (1 - e^{-Rt/L})$$

$$v_R = E \left(1 - e^{-\frac{Rt}{L}} \right)$$

$$v_L = E \cdot e^{-Rt/L}$$

C-C Tsai

8


Time Constant

- $\tau = L/R$, units are seconds
- The larger the inductance
 - The longer the transient
- The larger the resistance
 - The shorter the transient
- As R increases
 - Circuit looks more and more resistive
 - If R is much greater than L , the circuit looks purely resistive

$$i = \frac{E}{R} (1 - e^{-t/\tau})$$

$$v_L = E \cdot e^{-t/\tau}$$

$$v_R = E (1 - e^{-t/\tau})$$

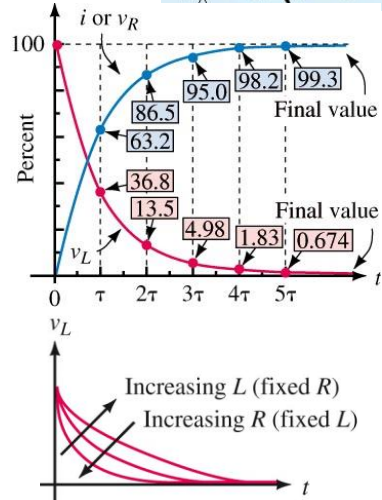

C-C Tsai



9

Example: RL Transients

- Given $E=50V$, $R=10\Omega$, and $L=2H$, determine $i(t)$.

$$\tau = L/R = 0.2s$$
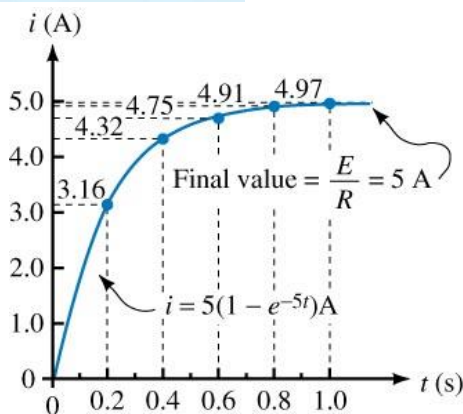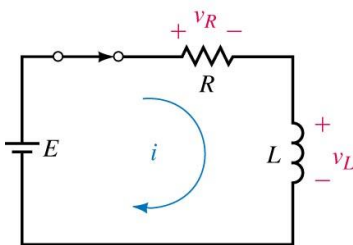
$$i(t) = \frac{E}{R} (1 - e^{-Rt/L}) \quad \text{or} \quad i = \frac{E}{R} (1 - e^{-t/\tau})$$



C-C Tsai


10

Example: RL Transients

- Given $E=50\text{V}$, $R=10\Omega$, and $L=2\text{H}$, determine $i(t)$.

$$\tau = L/R = 0.2\text{s}$$

$$v_L = E \cdot e^{-t/\tau}$$

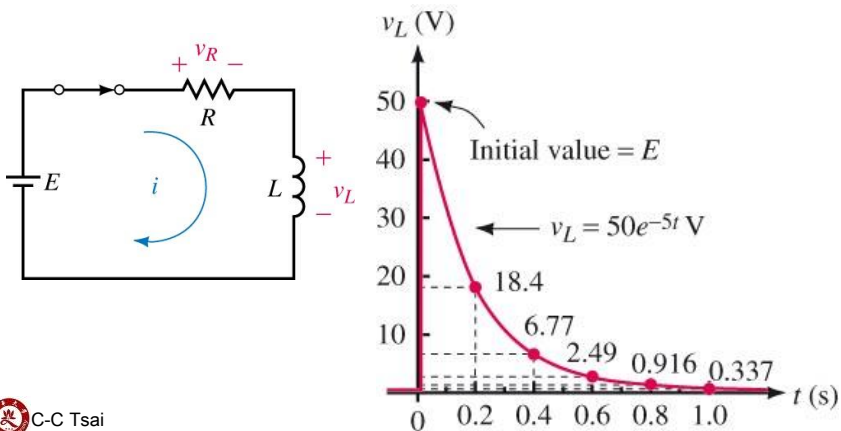


C-C Tsai

11

Interrupting Current in an Inductive Circuit

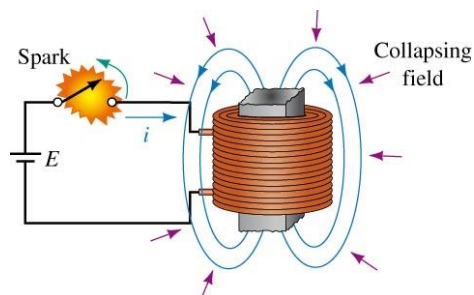- When switch opens in an RL circuit
 - Energy is released in a short time
 - This may create a large voltage
 - Induced voltage is called an inductive kick
- Opening of inductive circuit may cause **voltage spikes of thousands of volts**




C-C Tsai

12

Interrupting a Circuit

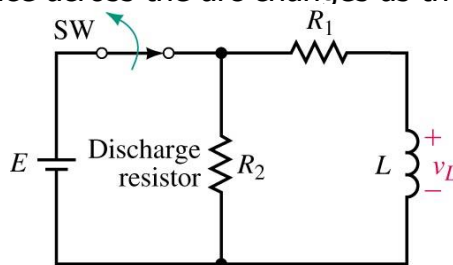
- Switch flashovers are generally undesirable
 - They can be controlled with proper engineering design
- These large voltages can be useful
 - Such as in **automotive ignition systems**
- It is not possible to completely analyze such a circuit
 - Resistance across the arc changes as the switch opens



C-C Tsai


13

Example: Interrupting a Circuit

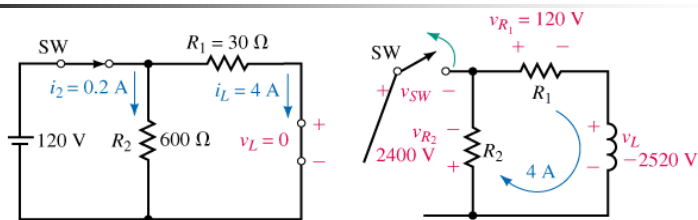

(a) Circuit just before the switch is opened

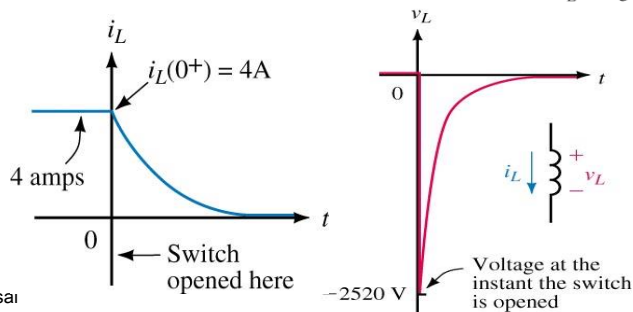(b) Circuit just after SW is opened. Since coil voltage polarity is opposite to that shown, v_L is negative




C-C Tsai


14

Inductor Equivalent at Switching

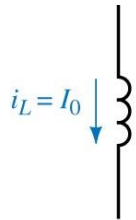- Current through an inductor
 - Same after switching as before switching
- An inductance with an initial current
 - Looks like a current source at instant of switching
- Its value is value of current at switching



(a) Current at switching

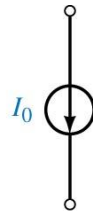

(b) Current source equivalent



15

De-energizing Transients

- If an inductor has an initial current I_0 , equation for **current** becomes

$$i = I_0 e^{-t/\tau'}$$

- $\tau' = L/R$. R equals total resistance in discharge path
- **Voltage across inductor** goes to zero as circuit de-energizes

$$v_L = V_0 e^{-t/\tau'}$$


- **Voltage across any resistor** is product of current and that resistor. Voltage across each of resistors goes to zero

$$v_R = R \cdot I_0 e^{-t/\tau'}$$




16


De-energizing Transients

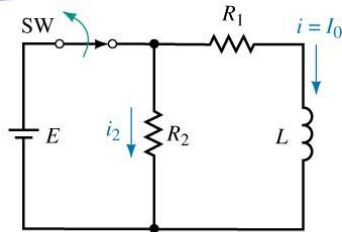

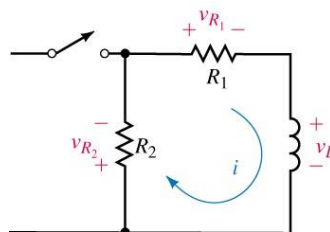(a) Immediately before the switch is opened




(b) Decay circuit

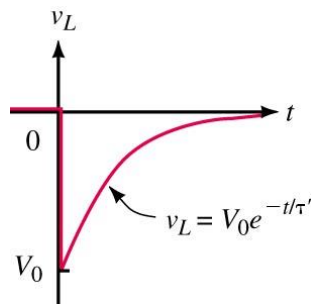


More Complex Circuits

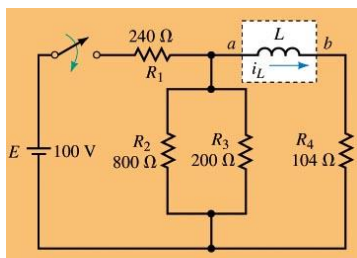- For complex circuits
 - Determine **Thévenin equivalent** circuit using inductor as the load
 - R_{Th} is used to determine time constant
 - $\tau = L/R_{Th}$
 - E_{Th} is used as source voltage




(a) Circuit

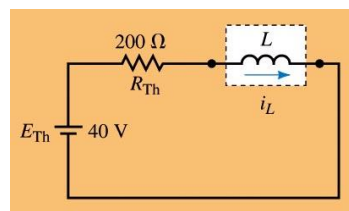


(b) Thévenin equivalent

Example1: More Complex Circuits

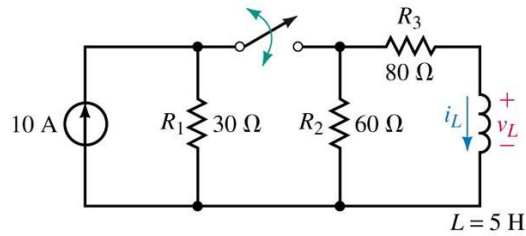


Switch is closed

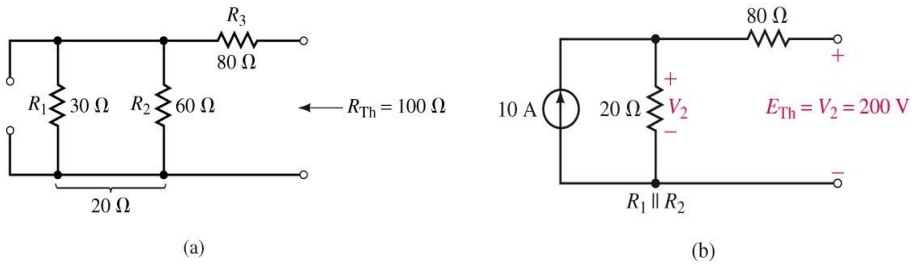


Example1: More Complex Circuits

Switch is closed (Cont'd)

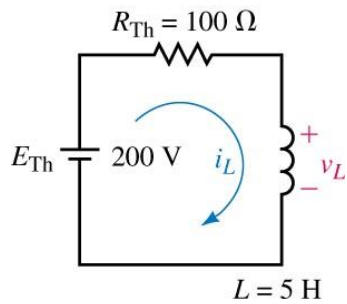


(a) Thévenin equivalent of Figure 14-24

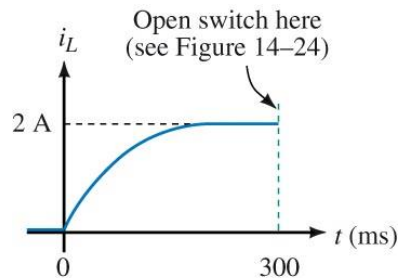


(b)


Example1: More Complex Circuits

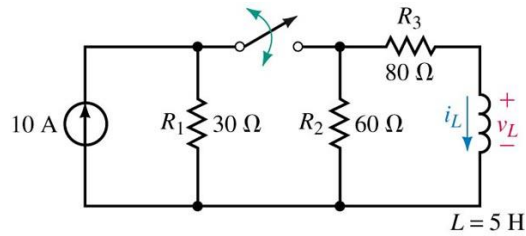

Switch is opened

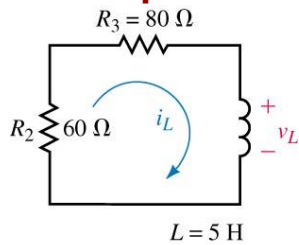

(a) Decay circuit

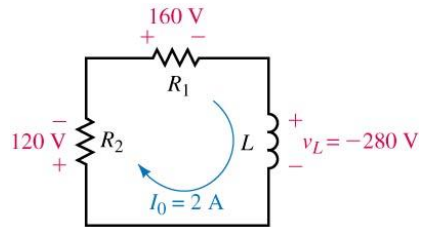


(b) As it looks immediately after the switch is opened. KVL yields $v_L = -280 \text{ V}$




21

Example1: More Complex Circuits

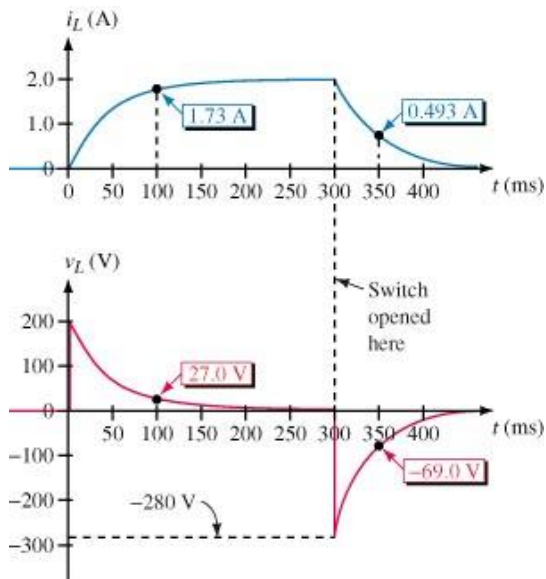


22



Example2: More Complex Circuits

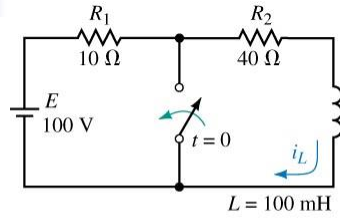

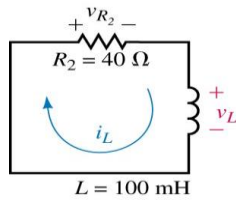
(a) Steady state current with the switch open is $\frac{100\text{ V}}{50\ \Omega} = 2\text{ A}$



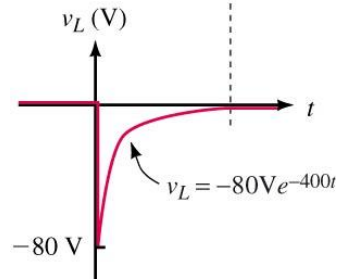
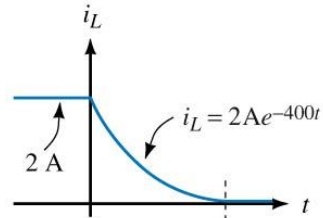
(b) Decay circuit
 $\tau = \frac{L}{R_2} = 2.5\text{ ms}$



Transient Analysis Using Computers

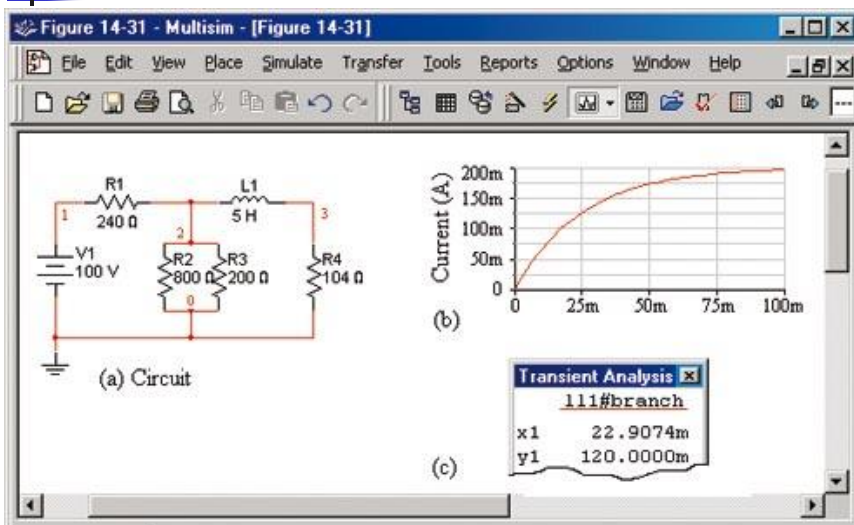


Transient Analysis Using Computers

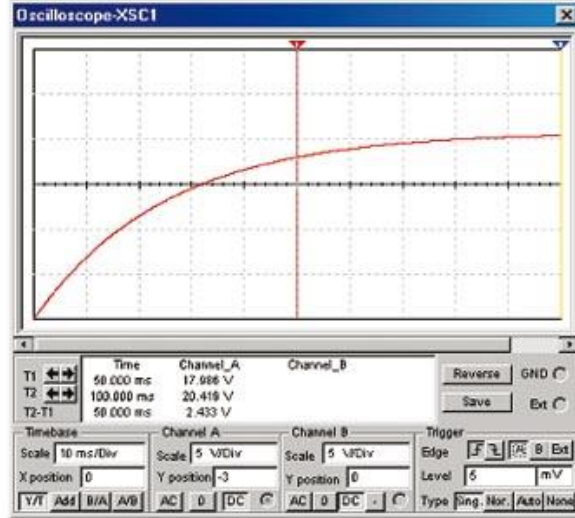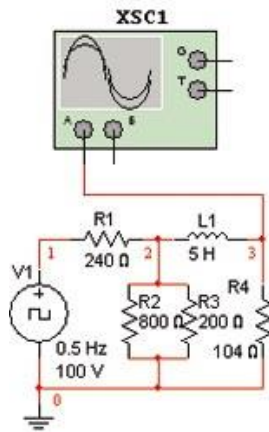

C-C Tsai

25

Problem: Determine i_L and v_L

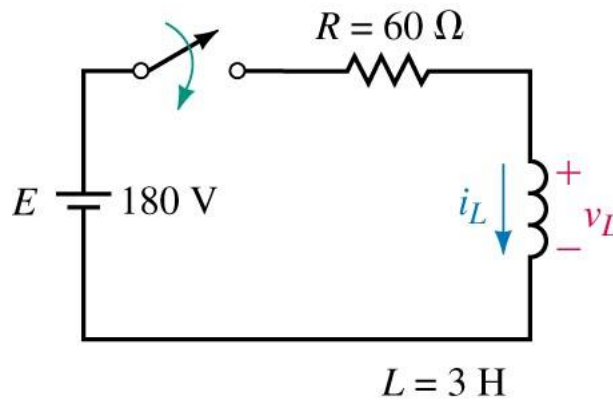

C-C Tsai

26



Problem: Determine i_L and v_L

