

# Chapter 05

## Series Circuits



Source: Circuit Analysis: Theory and Practice ©Delmar Cengage Learning



### Series Circuits

- Current is similar to water flowing through a pipe
  - **Current leaving** the element must be **the same** as the **current entering** the element
  - **Same current passes through every element of a series circuit**



C-C Tsai

## Kirchhoff's Voltage Law (KVL)

- The **algebraic sum** of the voltage that risers and drops around a **closed loop** is equal to **zero**

$$\sum E = 0 \quad \text{or} \quad E_T - V_1 - V_2 - V_3 - \dots - V_n = 0$$

- Another way of stating KVL is:
  - Summation of **voltage rises** is **equal to** the summation of **voltage drops** around a **closed loop**

$$E_T = V_1 + V_2 + V_3 + \dots + V_n$$

## Resistors in Series

- For a circuit with 3 resistors:  $E = V_1 + V_2 + V_3$


$$R_T = R_1 + R_2 + R_3$$

# Loading Effects


$$\text{loading effect} = \frac{\text{theoretical value} - \text{measured value}}{\text{theoretical value}} \times 100\%$$



# Multisim

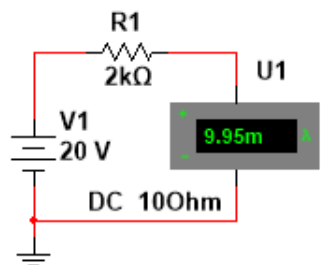

$$LD = (10m - 9.95m) / 10m = 0.5\%$$

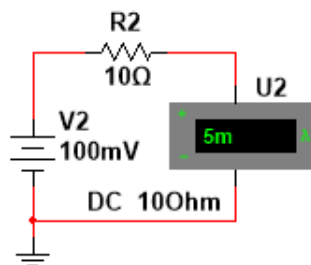

$$LD = (10m - 5m) / 10m = 50\% \quad \text{即 Loading effect}$$



## Kernel abilities

---

1. What is **total resistance  $R_t$**  of resistors  $R_1 \sim R_n$  in **series**? Please give an example.
2. What is **KVL**? Please give an example.
3. What is **voltage divider for a series circuit**? Please give an example. (larger resistance larger voltage)
4. What is **loading effect of measuring current**? Please give an example. (depending on the internal resistance of a current meter)