


# Chapter 07

## Series-Parallel Circuits

 Source: Circuit Analysis: Theory and Practice ©Delmar Cengage Learning



### Analysis of Series-Parallel Circuits

Rules for analyzing series and parallel circuits apply:

- **Same current** occurs through all series elements
- **Same voltage** occurs across all parallel elements
- **KVL and KCL** apply for all circuits


Steps to simplify a circuit:

- Redraw complicated circuits **showing the source at the left-hand side** and then label all nodes
- Simplify recognizable combinations of components
- Determine **equivalent resistance  $R_T$**  and solve for the total current
- Label polarities of voltage drops on all components
- **Calculate how currents and voltages split between elements** in a circuit
- Verify your answer by taking a different approach

 C-C Tsai

2
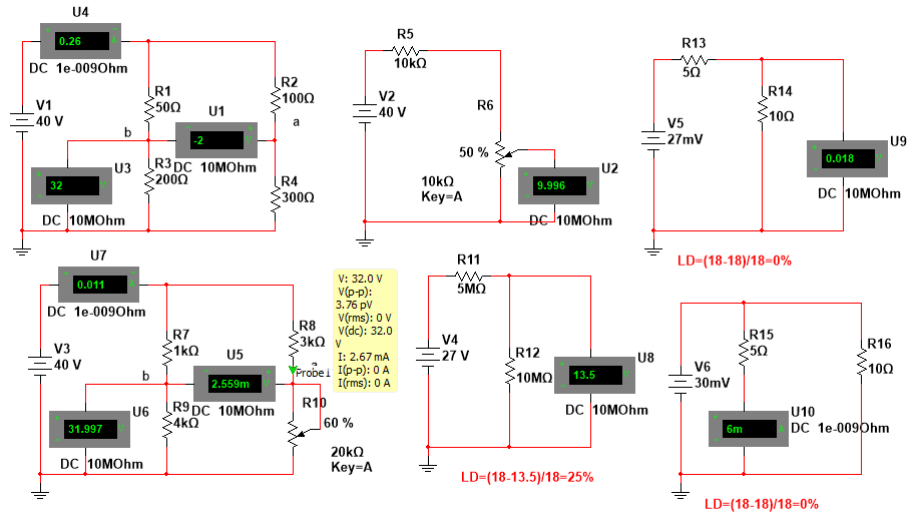
## Get Voltages and currents Using Multisim



## Kernel abilities

1. Can recognize which parts are in series or parallel for a series-parallel circuit.
2. Can compute the total resistance  $R_t$  of resistors  $R_1 \sim R_n$  in series-parallel.
3. Can recognize KVL and KCL for applying a series-parallel circuit.
4. Can recognize the voltage divider and current divider for applying a series-parallel circuit.
5. Can recognize the loading effect for measuring voltage and current.