

# Chapter 08 & 09

## Methods of Circuit Analysis



Source: Circuit Analysis: Theory and Practice ©Delmar Cengage Learning



## Outline


- **Source Conversion**
- **Nodal Analysis**
- **Bridge Networks**
- **Superposition Theory**
- **Thévenin's Theory**
- **Maximum Power Transfer**
- **Millman's Theorem**




C-C Tsai
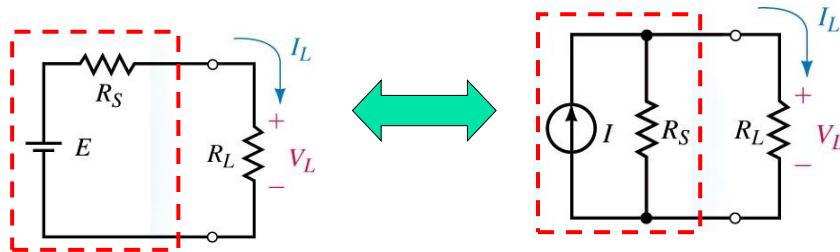
## Current and Voltage Sources Exchange

- Sources are only equivalent external to terminals


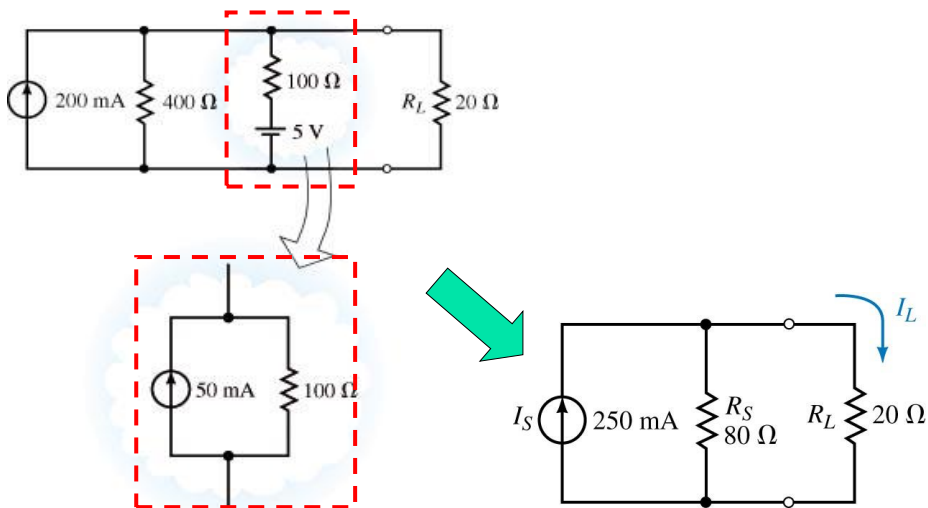
## Example2: Current Sources in Parallel and Series



# Nodal Analysis

**Step0: Assign a reference node** within circuit and indicate node **as ground**

- Convert voltage sources to current sources
- Arbitrarily assign a current direction to each branch where there is no current source

**Step1: Assign voltages  $V_1, V_2,$  etc. to remaining nodes**

**Step2: Apply KCL to all nodes** except reference node


**Step3: Solve resulting equations for voltages**



5

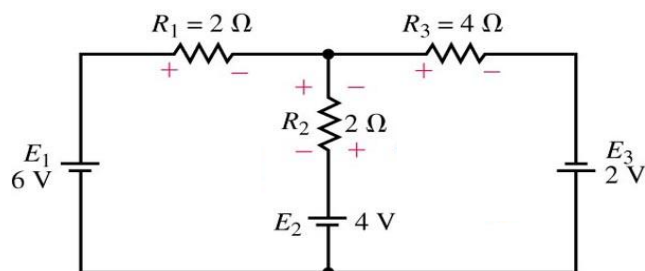
## Example0: Nodal Analysis

- Assign voltage at node, then using KVL  
 **$(V_1-6)/2 + (V_1-4)/2 + (V_1-(-2))/4 = 0$**



6

## Example3: Nodal Analysis

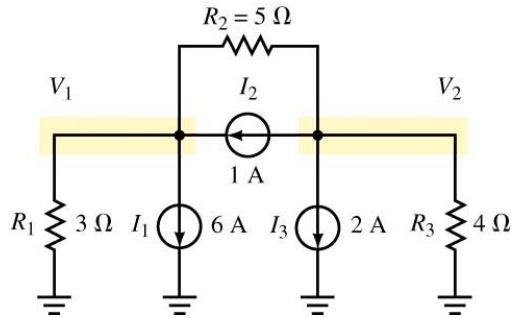

Using KCL for nodes  $V_1$  and  $V_2$

$$V_1/3 + (V_1 - V_2)/5 + 6 = 1$$

$$V_2/4 + (V_2 - V_1)/5 + 2 + 1 = 0$$




7

## Bridge Networks

- **Balanced bridge:**

$$30 * 240 = 60 * 120$$

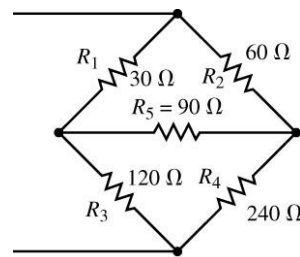
$$R_1 R_4 = R_2 R_3 \text{ and } I_{R_5} = 0$$



- **Unbalanced bridge:**


$$20 * 80 \neq 40 * 60$$
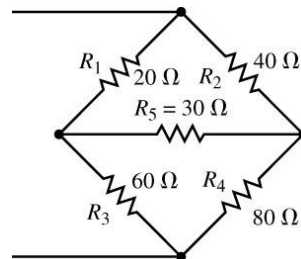
$$R_1 R_4 \neq R_2 R_3 \text{ and } I_{R_5} \neq 0$$



8

## Example: Bridge Networks


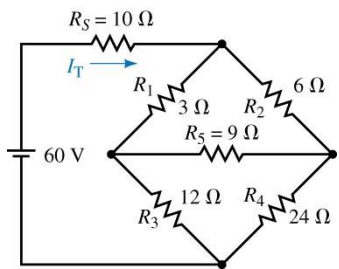


- **Balanced bridge:**

**$3 \cdot 24 = 6 \cdot 12$**

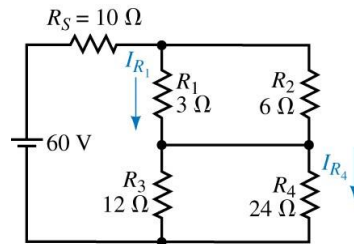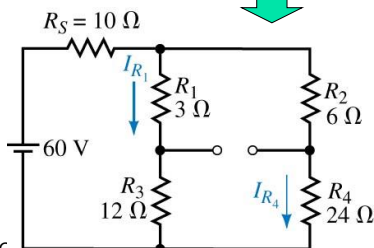**$R_1 R_4 = R_2 R_3$  and  $I_{R_5} = 0$**


- $R_5$  can be replaced with **an open circuit** or **a short circuit**.



9

## Problem 14

**Determine the voltage  $V_{ab}$**

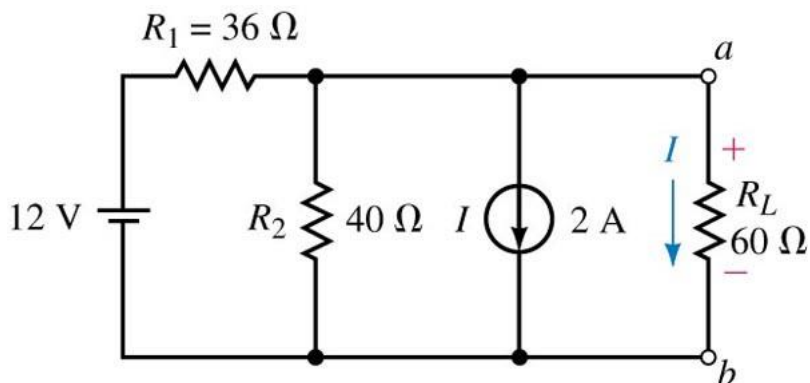


10

# Superposition Theorem

- **Total current through** or **voltage across** a resistor or branch
  - **Determine by adding effects due to each source acting independently**
- **Replace a voltage source with a short**
- **Replace a current source with an open**
- Find results of branches using each source independently
  - **Algebraically combine results**

## Example: Superposition Theorem


**Find  $I_L$**

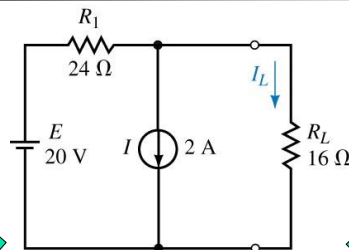

$$I_L = I_{L(1)} + I_{L(2)} = -0.7A$$

$$P_{RL} = 7.84W$$

$$\neq P_{RL(1)} + P_{RL(2)} = 27.04W$$

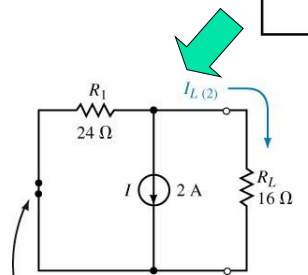


**Replace a voltage source with a short**

$$I_{L(2)} = -2 * 24 / 40 = -1.2A$$

$$P_{(2)} = 23.04W$$

$$I_{L(1)} = 20 / 40 = 0.5A$$


$$P_{(1)} = 4W$$

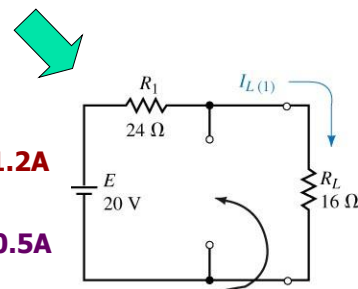

**Replace a current source with an open**
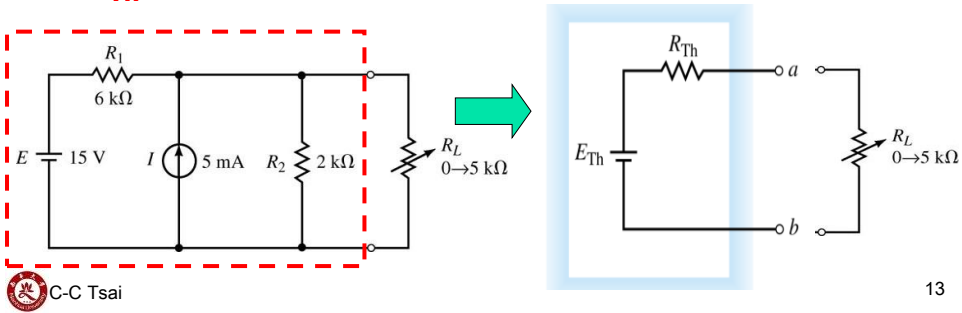
# Thévenin's Theorem

- Any linear bilateral network can be reduced to a **simplified two-terminal circuit with a single voltage source in series with a single resistor**
- Voltage source: Thévenin equivalent voltage,  $E_{Th}$ .
- Series resistance: Thévenin equivalent resistance,  $R_{Th}$ .




C-C Tsai

13

## Example 2: Thévenin's Theorem

Calculate the current through  $R_L$


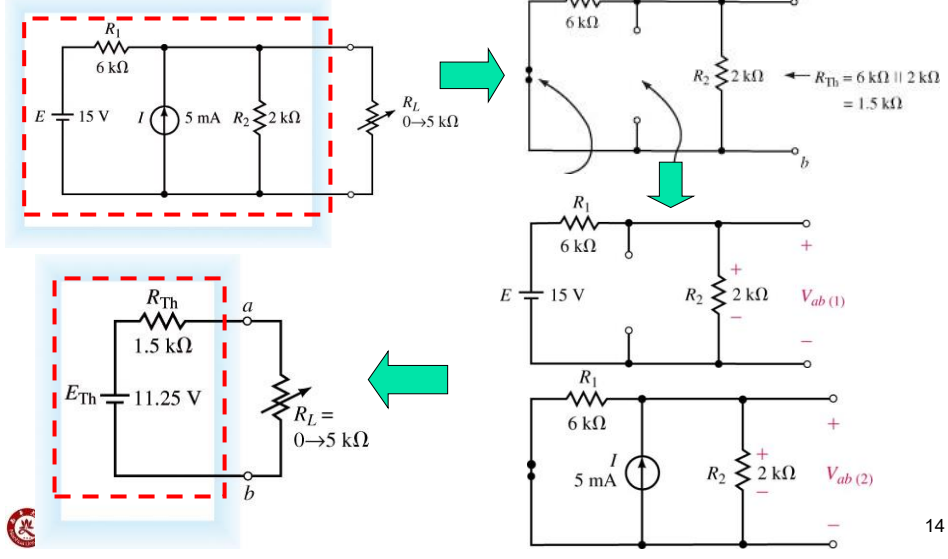


C-C Tsai

14
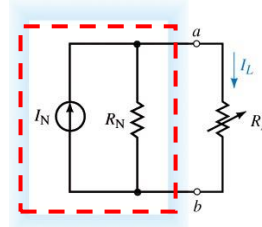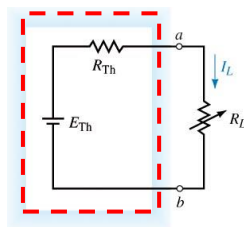
# Maximum Power Transfer

- **A load resistor will receive maximum power** from a circuit when its resistance is the same as the Thévenin (or Norton) equivalent resistance
- Calculate maximum power delivered by source to load by using  $P = V^2/R$
- **Voltage across load is one half of Thévenin equivalent voltage**
- Current through load is one half of Norton equivalent current





C-C Tsai

15
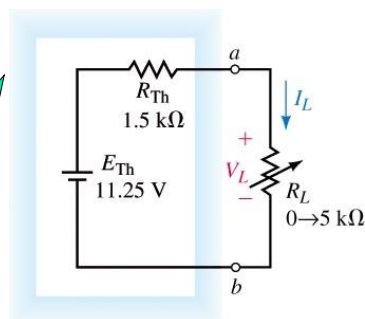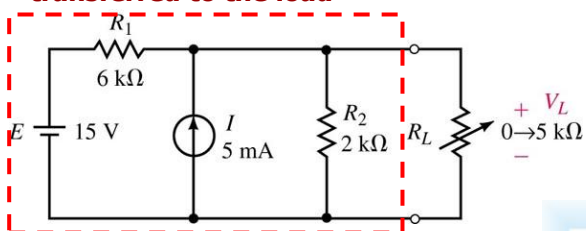
# Example: Maximum Power Transfer

Determine the **load resistance** to ensure that **maximum power is transferred to the load**




C-C Tsai

16
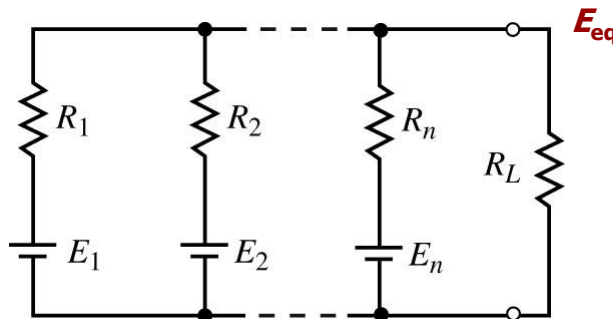
# Millman's Theorem

- Used to simplify circuits that have
  - Several parallel-connected branches containing a voltage source and series resistance
  - Current source and parallel resistance
  - Combination of both :  $E_{eq} = I_{eq}R_{eq}$




C-C Tsai


17

# Example: Millman's Theorem

- We can simplify a circuit as shown:

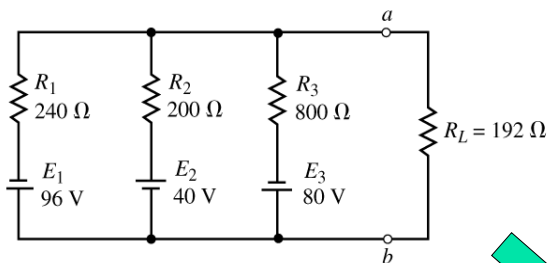
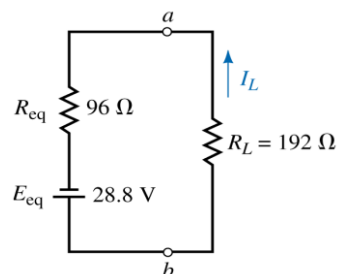
$$V_{ab} = \frac{(-96/240 + 40/200 - 80/800 + 0/192)}{(1/240 + 1/200 + 1/800 + 1/192)}$$




C-C Tsai


18
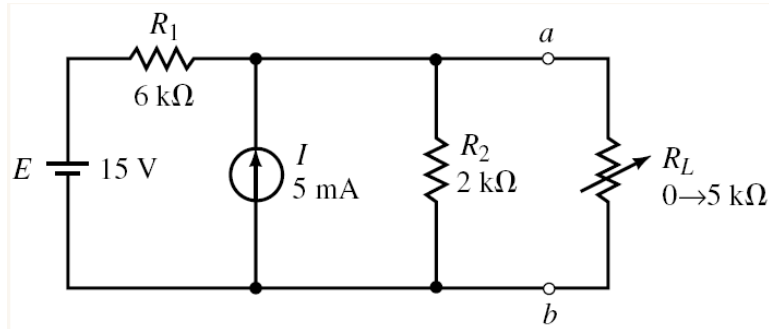
# Circuit Analysis Using Multisim

- Find both the Thévenin and the Norton equivalent circuits external to the load resistor in the circuit shown



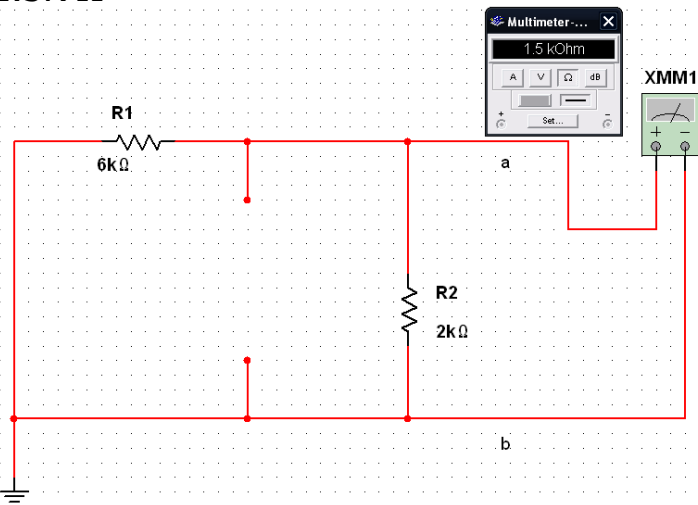- Use a multimeter to find the equivalent resistance 1.5K Ω





- Use a multimeter to find the open circuit voltage 11.25V

