

Chapter 08

Methods of Analysis 分析方法



C-C Tsai Source: Circuit Analysis: Theory and Practice ©Delmar Cengage Learning

Outline



- **Source Conversion** 電源轉換
- **Mesh Analysis** 迴路分析法
- **Nodal Analysis** 節點分析法
- **Delta-Wye (Δ -Y) Conversion**
 Δ -Y轉換
- **Bridge Networks** 電橋網路



C-C Tsai

Using Source Conversions

電源轉換

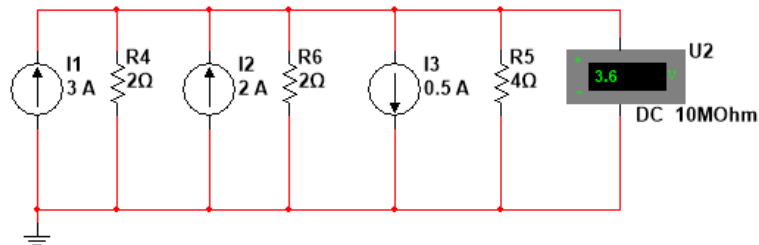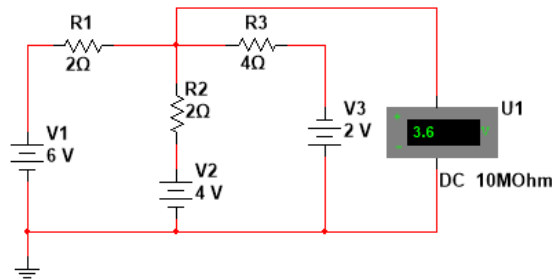

Branch Current Analysis

分支電流分析法

Used for circuits having more than one source

Step0: Arbitrarily Assume all the current I_1, I_2, \dots

任意指定所有分支電流任一方向 I_1, I_2, \dots

Step1: Label polarities of the voltage drops across all resistors

依指定電流方向來標示每個電阻的電壓+、-端

Step2: Write KVL around all loops

列出所有閉迴路之KVL式子

Step3: Apply KCL at enough nodes so all branches have been included

列出所有節點之KCL式子

Step4: Solve resulting equations 解聯立方程式

Mesh Analysis

迴路分析法

Step0: Arbitrarily assign a clockwise current to each interior closed loop (Mesh)

對每一個閉迴路任意指定電流方向 I_1, I_2, \dots

Step1: Indicate voltage polarities across all resistors


依指定電流方向來標示每個電阻的電壓+、-端

Step2: Write KVL equations

列出所有閉迴路之KVL式子

Step3: Solve resulting simultaneous equations

解聯立方程式，求電流 I_1, I_2, \dots

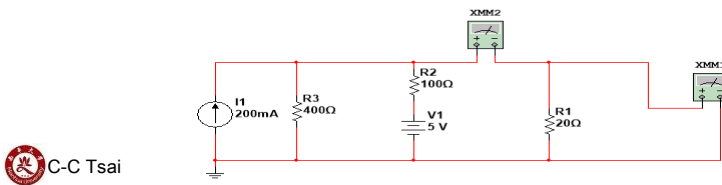


C-C Tsai

5

Mesh Analysis

迴路分析法

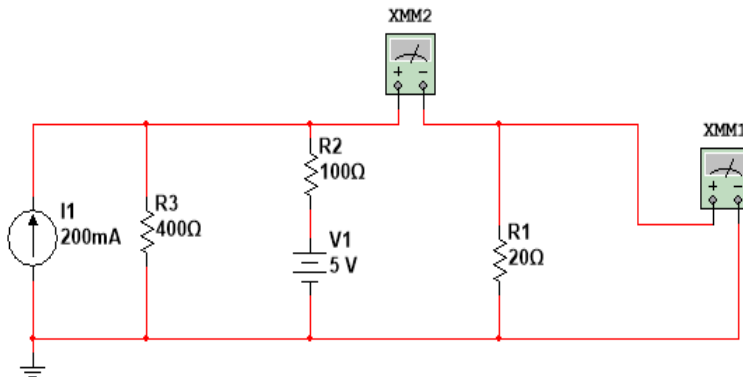

C-C Tsai

6

Nodal Analysis

節點分析法

Step0: Assign a reference node within circuit and indicate node **as ground** 區分一般節點與參考節點(接地)

Assign voltages V_1, V_2, \dots to nodes
指定每個節點及標示電壓 V_1, V_2, \dots

Step1: Arbitrarily assign a current direction to each branch at a node.


對每一節點定任意標示其分支電流方向

Step2: Apply KCL to all nodes except reference node 列出每一節點(接地點除外)之KCL式子

Step3: Solve resulting equations for voltages
解聯立方程式，求電壓 V_1, V_2, \dots

Nodal Analysis

節點分析法

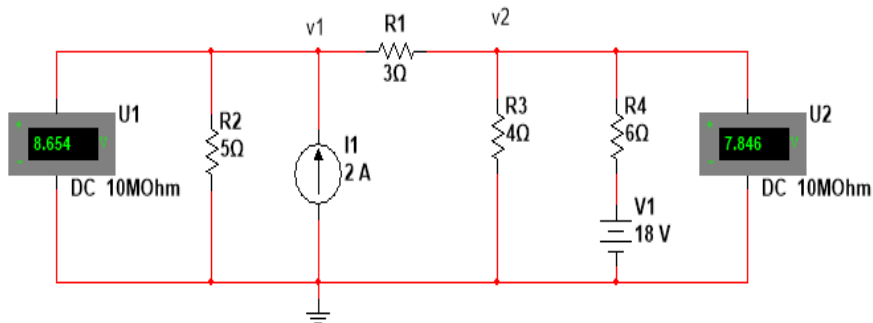


Delta-Wye (Δ -Y) Conversion

Δ 型連接 轉換為 Y型連接

對應左右電阻相乘 除以 所有電阻相加

$$R_1 = (R_C * R_B) / (R_A + R_B + R_C)$$
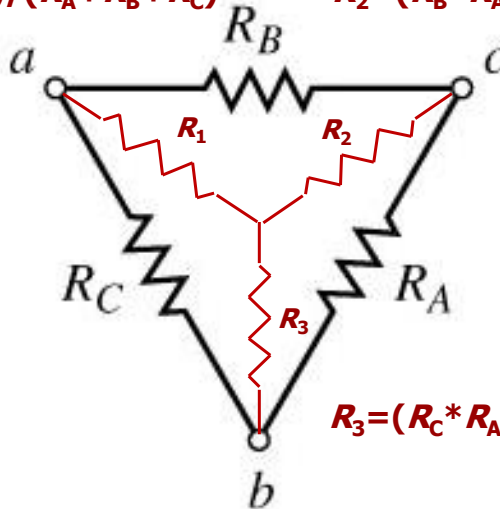
$$R_2 = (R_B * R_A) / (R_A + R_B + R_C)$$




$$R_3 = (R_C * R_A) / (R_A + R_B + R_C)$$

Delta-Wye (Δ -Y) Conversion

Δ 型連接 轉換為 Y型連接

兩兩電阻相乘後加起來 除以 對應電阻
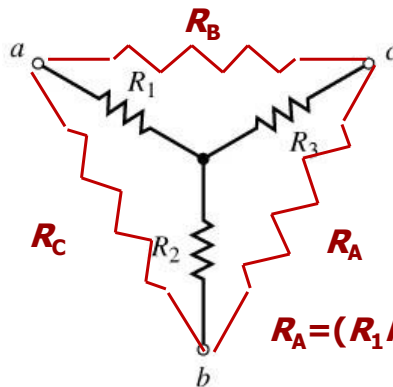
$$R_B = (R_1 R_2 + R_2 R_3 + R_1 R_3) / R_2$$



$$R_A = (R_1 R_2 + R_2 R_3 + R_1 R_3) / R_1$$

$$R_C = (R_1 R_2 + R_2 R_3 + R_1 R_3) / R_3$$

Bridge Networks

電橋網路



- **Balanced bridge:** 平衡電橋條件

$$R_1 R_4 = R_2 R_3 \text{ and } I_{R_5} = 0 \text{ and } V_{ab} = 0$$

R_5 可視為開路或短路

- **Unbalanced bridge:** 不平衡電橋條件
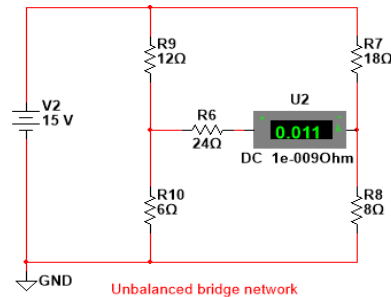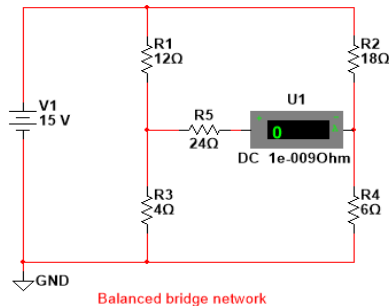
$$R_1 R_4 \neq R_2 R_3 \text{ and } I_{R_5} \neq 0$$



Kernel abilities

1. Can use **Voltage and Current conversion** for analyze a circuit
2. Can use **Mesh Analysis** for solving the unknown voltage and current of a circuit.
3. Can use **Nodal Analysis** for solving the unknown voltage and current of a circuit.
4. Can use **Delta-Wye (Δ -Y) Conversion** for solving the unknown voltage and current of a circuit.
5. Can recognize a Bridge circuit whether is **balanced** or **unbalanced** and solve the unknown voltage and current.