



Lab-02

Basic Logic Gates

Chia-Chun Tsai

Objectives



- Understand a module of digital system and all the components on the module
- Understand basic logic gates, **NOT**, **AND**, **OR**, **NAND**, **NOR**, **XOR**, and **XNOR** and their **truth tables**.
- Measure the voltage of logic **“1”** or **“H”** and the voltage of logic **“0”** or **“L”**.
- Understand two major digital IC families, **TTL** and **CMOS**.


Chia-Chun Tsai

2

Module for Practice of Digital System




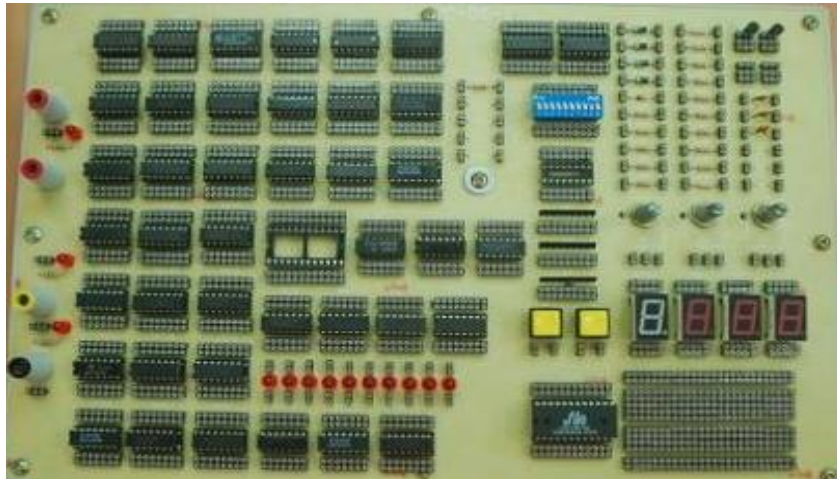
TTL/CMOS ICs, Resistors, Capacitors, LEDs, SW, 7-segment Display, Push-button, and IC slots.



Chia-Chun Tsai

3

Breadboard

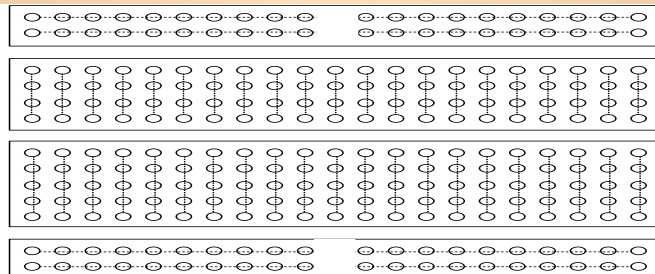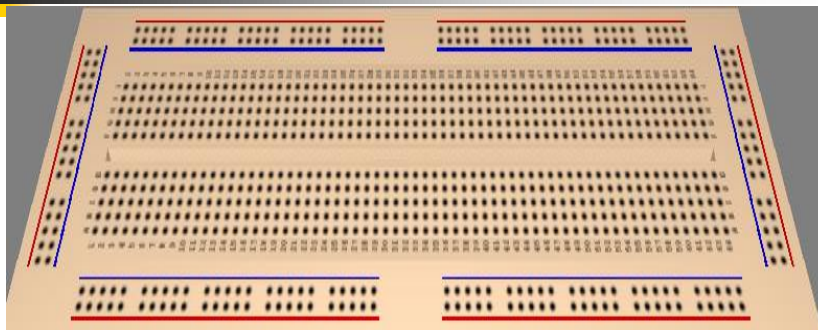



Chia-Chun Tsai

4

Resistor and Resistor Pack





Resistor2_4.7kOhm

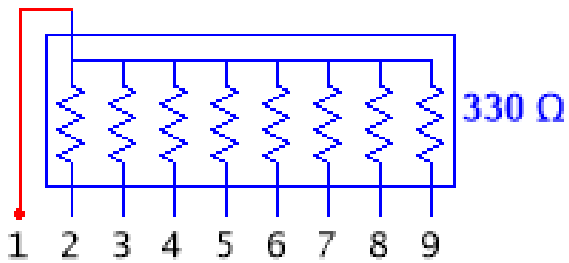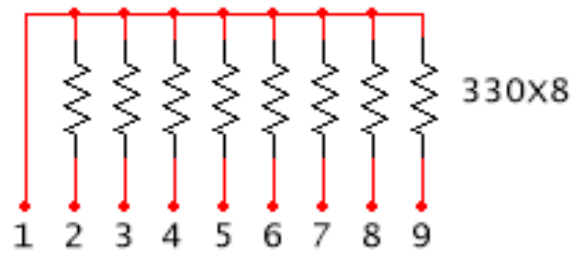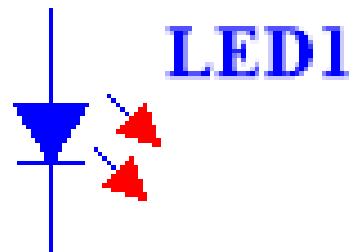

Chia-Chun Tsai

5



LED (Light Emitting Diode)



Chia-Chun Tsai

6

IC (Integrated Circuit)

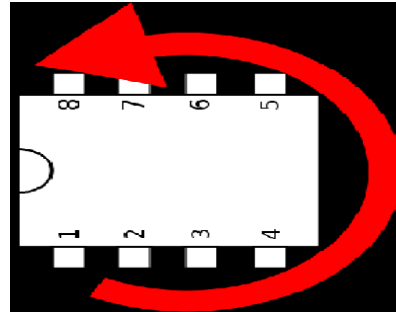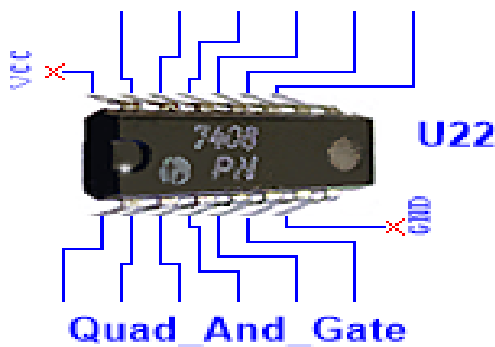

Chia-Chun Tsai

7

Classification for Logic Gates



- **Basic Logic Gates** have NOT, AND, OR, NAND, NOR, and XOR gates.
- **Basic Logic Gates** have two kinds of major circuits:

TTL (Transistor-Transistor Logics)

74xx series: 7400, 7402, 7404, 7486, ...

CMOS-FET (Compliment Metal-Oxide-Semiconductor Field-Effect-Transistor Logics)

40xx series: 4001, 4010, 4011, 4049, ...

Chia-Chun Tsai

8

Integrated Circuits (ICs)



7400	7402	74147	7408	7474	4560		7476	7476
7411	7417	74165	74125	4518	7483			
7404	74151	7442	4011	7474	7490			
7410	7447	4049	2732	4561	74164	4070		
7432	74148	4010	4071	4001	7486	74155		
7409	74138	4013						
7490	4081	4027	7414	74121	4511		6116	


Open collector: 7409, 7417

Extra ICs: 555、7485、7493、74190、74198、4017

Chia-Chun Tsai

9


TTL ICs – Basic Gates

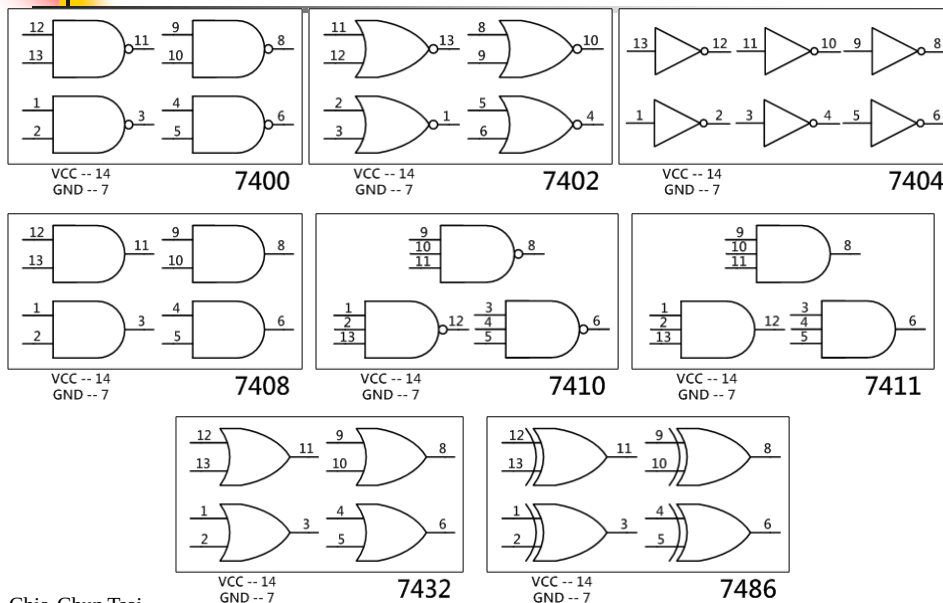

Chia-Chun Tsai

10


CMOS ICs – Basic Gates

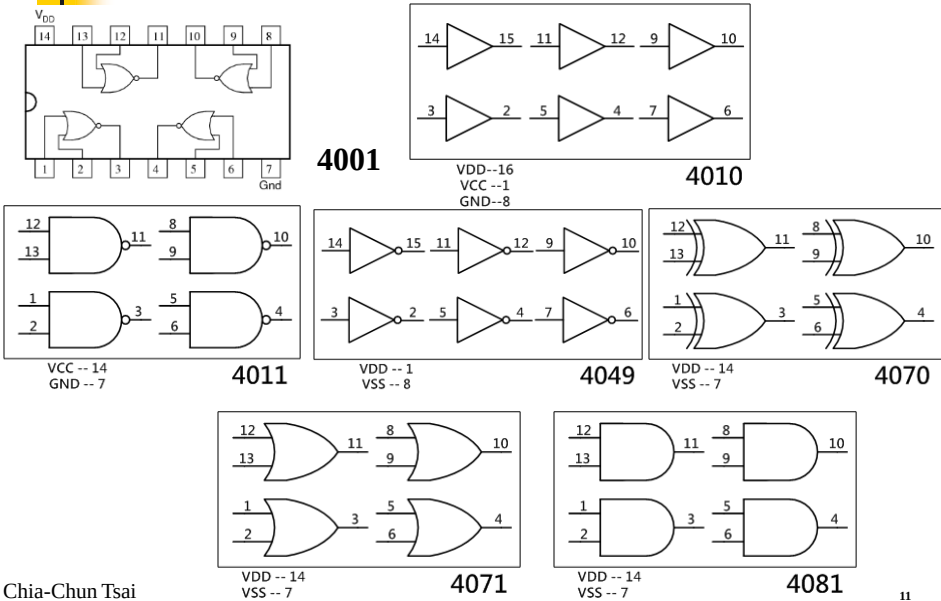

Chia-Chun Tsai

11

IC Types and Pins

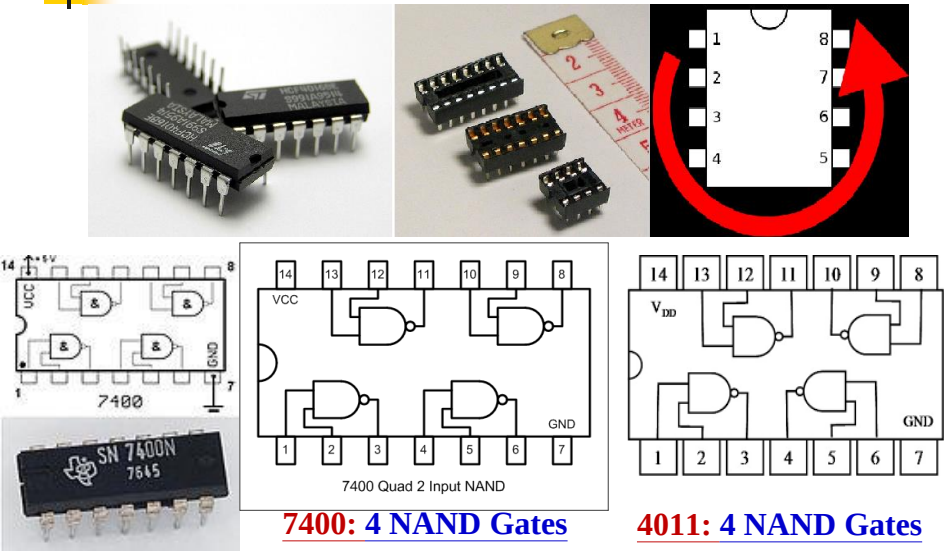

Chia-Chun Tsai

12

TTL/CMOS Logics



Power supply

TTL ICs: VCC 5V GND 0V

CMOS IC: VDD 3~18V VSS 0V

	TTL (VCC=5V)	CMOS (VDD=5V)	Logic
V_{IH}	$\geq 2.0V$	$\geq 0.7 VDD$ $\geq 3.5V$	1
V_{IL}	$\leq 0.8V$	$\leq 0.3 VDD$ $\leq 1.5V$	0
V_{OH}	$\geq 2.4V$	$\approx VDD$ $\approx 5V$	1
V_{OL}	$\leq 0.4V$	$\approx VSS$ $\approx 0V$	0


Chia-Chun Tsai

13

NOT Gate



A	Y = /A
0	1
1	0

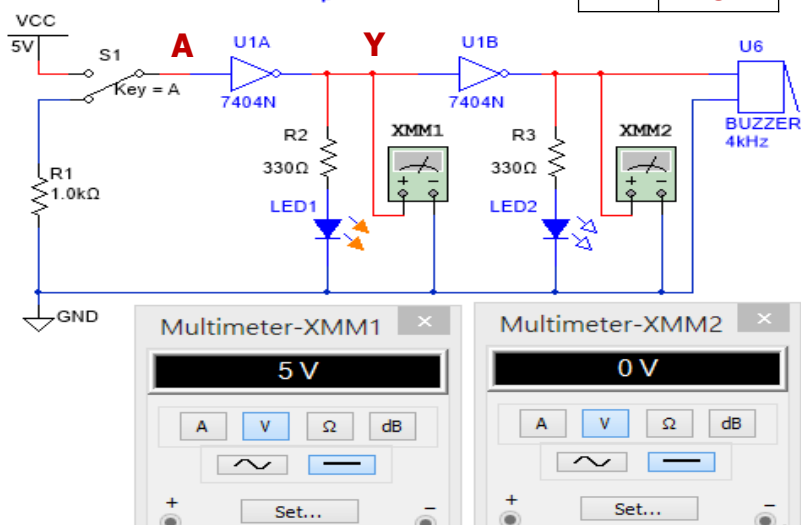


Chia-C

14



NOT Gate

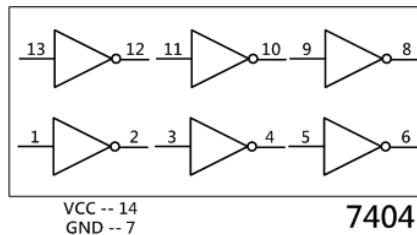

A	Y = /A
0	1
1	0

A	Y = /A
0V	4.41V
5V	0.15V

Every IC needs power supply

VCC pin-14 +5V

GND pin-7 0V



Chia-Chun Tsai

15



Transfer Voltage of NOT


Transfer voltage $V_{tr} = 2.561V$

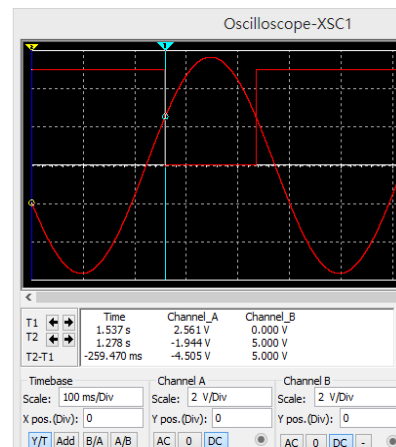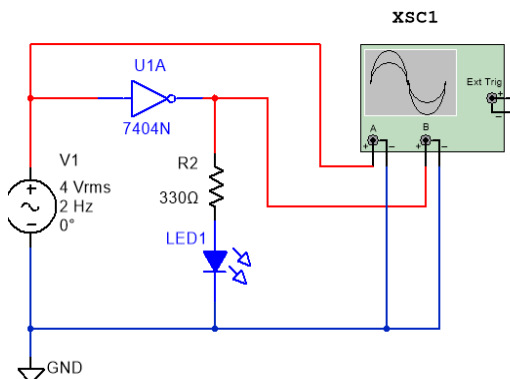



Chia-Chun Tsai

16

AND Gate

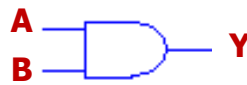


A	B	Y=AB
0	0	0
0	1	0
1	0	0
1	1	1

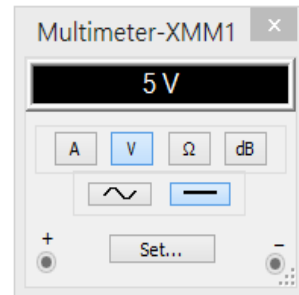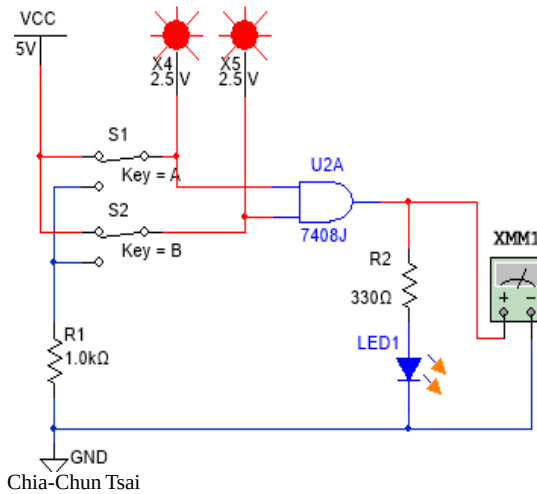

Chia-Chun Tsai

17

AND Gate

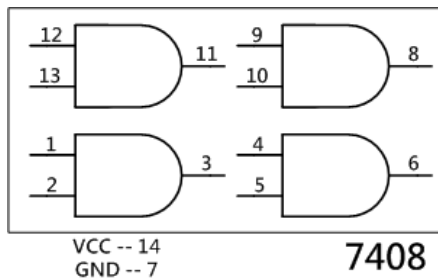

A	B	Y=AB
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Y=AB
0V	0V	0.15V
0V	5V	0.15V
5V	0V	0.15V
5V	5V	4.41V

The IC needs power supply

VCC pin-14 +5V

GND pin-7 0V

Chia-Chun Tsai

18

OR Gate

Chia-Chun Tsai

A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1

OR Gate

VCC -- 14
GND -- 7

7432

A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1

The IC needs power supply

VCC pin-14 +5V

GND pin-7 0V

A	B	Y=A+B
0V	0V	0.15V
0V	5V	4.41V
5V	0V	4.41V
5V	5V	4.41V

A	B	Y=/(AB)
0	0	1
0	1	1
1	0	1
1	1	0

Chia-Chun Tsai

VCC -- 14
GND -- 7

7400

A	B	Y=/(AB)
0	0	1
0	1	1
1	0	1
1	1	0

The IC needs power supply

VCC pin-14 +5V

GND pin-7 0V


A	B	Y=/(AB)
0V	0V	4.41V
0V	5V	4.41V
5V	0V	4.41V
5V	5V	0.15V

Chia-Chun Tsai

NOR Gate




A	B	$Y = \neg(A+B)$
0	0	1
0	1	0
1	0	0
1	1	0

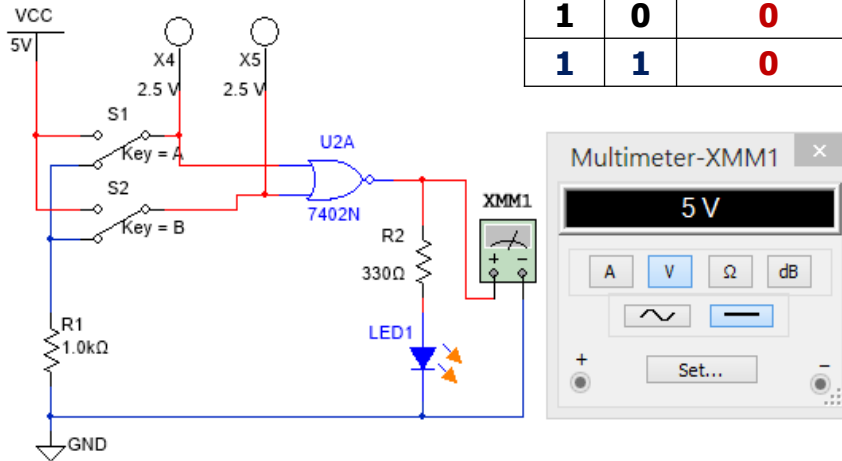

Chia-Chun Tsai

23

NOR Gate

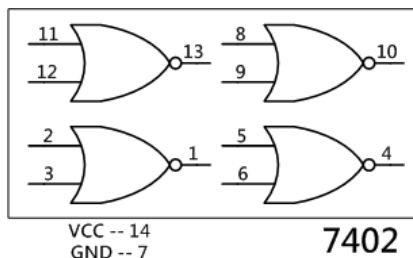

A	B	$Y = \neg(A+B)$
0	0	1
0	1	0
1	0	0
1	1	0

A	B	$Y = \neg(A+B)$
0V	0V	4.41V
0V	5V	0.15V
5V	0V	0.15V
5V	5V	0.15V

The IC needs power supply



VCC pin-14 +5V

GND pin-7 0V

Chia-Chun Tsai

24

XOR Gate

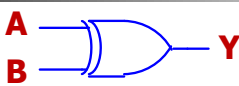
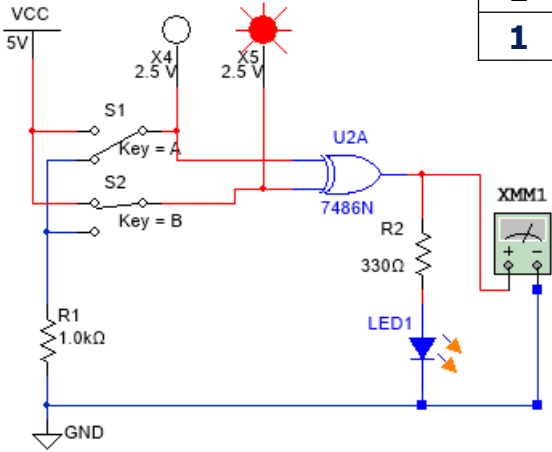



Chia-Chun Tsai

A	B	Y=A/B+B/A
0	0	0
0	1	1
1	0	1
1	1	0



XOR Gate

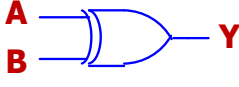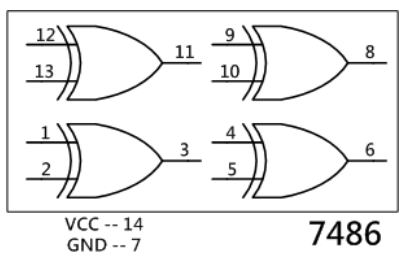VCC -- 14
GND -- 7

7486

A	B	Y=A/B+B/A
0	0	0
0	1	1
1	0	1
1	1	0

The IC needs power supply


VCC pin-14 +5V

GND pin-7 0V

A	B	Y=A/B+B/A
0V	0V	0.15V
0V	5V	4.41V
5V	0V	4.41V
5V	5V	0.15V



Experiment-1 NOT Gate

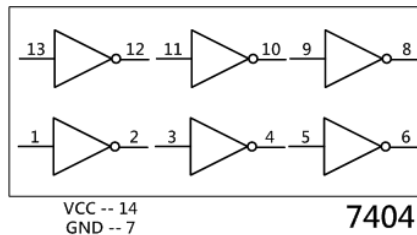

A	Y = /A
0	1
1	0

A	Y = /A
0V	____ V
5V	____ V

Every IC needs power supply


VCC pin-14 +5V

GND pin-7 0V

Chia-Chun Tsai

27

Experiment-2 AND Gate

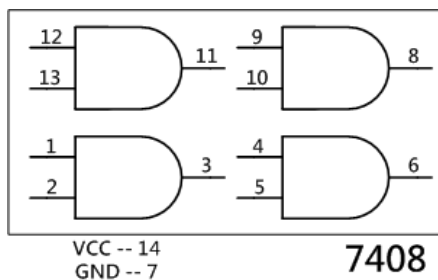

A	B	Y = AB
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Y = AB
0V	0V	____ V
0V	5V	____ V
5V	0V	____ V
5V	5V	____ V

The IC needs power supply



VCC pin-14 +5V

GND pin-7 0V

Chia-Chun Tsai

28

Experiment-3 OR Gate

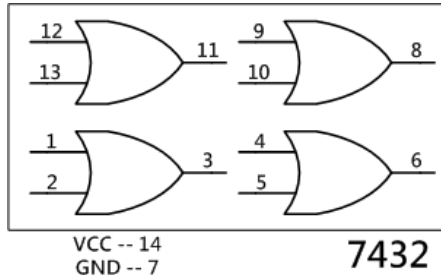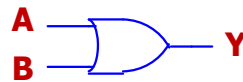

The IC needs power supply

VCC pin-14 +5V

GND pin-7 0V



A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1

A	B	Y=A+B
0V	0V	___ V
0V	5V	___ V
5V	0V	___ V
5V	5V	___ V

Chia-Chun Tsai

29

Experiment-4 NAND Gate

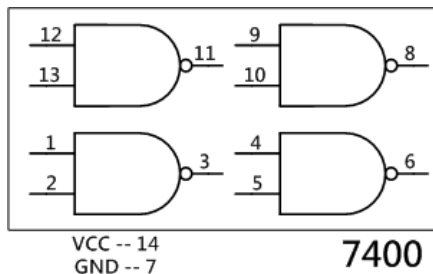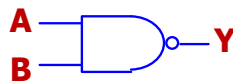

The IC needs power supply

VCC pin-14 +5V

GND pin-7 0V


A	B	Y=/(AB)
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Y=/(AB)
0V	0V	___ V
0V	5V	___ V
5V	0V	___ V
5V	5V	___ V

Chia-Chun Tsai

30

Experiment-5 NOR Gate

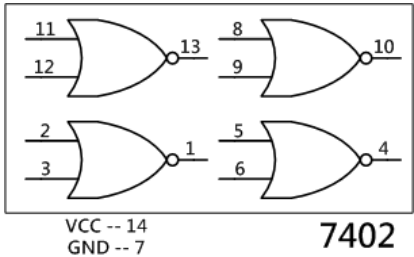

A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0



A	B	$Y = \overline{A+B}$
0V	0V	___ V
0V	5V	___ V
5V	0V	___ V
5V	5V	___ V

The IC needs power supply
VCC pin-14 +5V
GND pin-7 0V

Chia-Chun Tsai

31

Experiment-6 XOR Gate

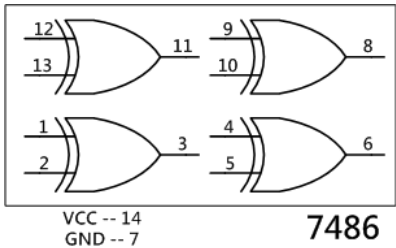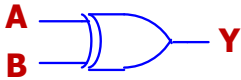

A	B	$Y = A/B + B/A$
0	0	0
0	1	1
1	0	1
1	1	0

A	B	$Y = A/B + B/A$
0V	0V	___ V
0V	5V	___ V
5V	0V	___ V
5V	5V	___ V

The IC needs power supply
VCC pin-14 +5V
GND pin-7 0V

Chia-Chun Tsai

32