



Lab-06

Application of Logic Gates

Chia-Chun Tsai

Objectives




- Understand to use **basic gates** to form a **digital system** what you want.
- Implement an **e-Dice** using basic gates.
- Implement an **e-Key** using XOR gates.
- Implement an **e-Key** using 4-bit comparator.

Chia-Chun Tsai

2


e-Dice based on 3-input NANDs

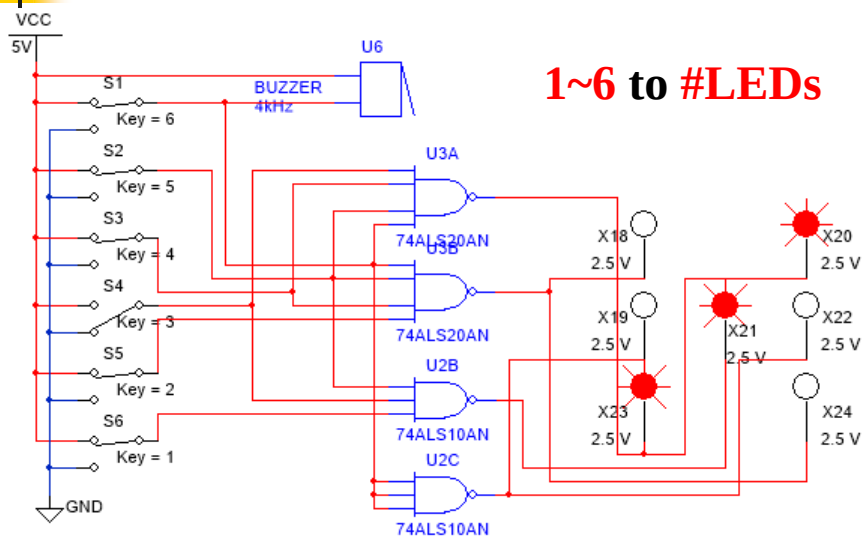

Chia-Chun Tsai

3

e-Key based on an XOR Gate

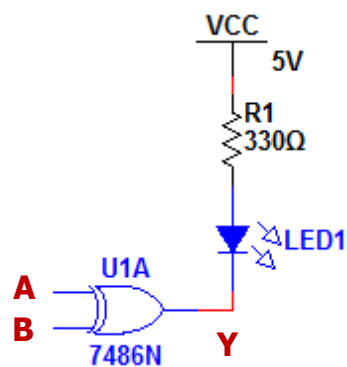


A	B		Y	LED1
0	0	A=B	0	ON
0	1	A≠B	1	OFF
1	0	A≠B	1	OFF
1	1	A=B	0	ON

Chia-Chun Tsai

4

Odd Parity based on XORs

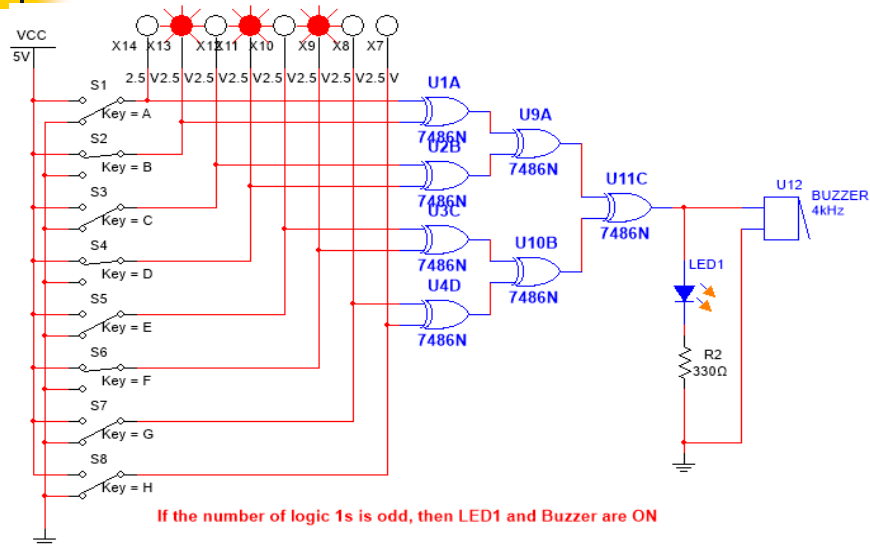


If the number of logic 1s is odd, then LED1 and Buzzer are ON

Chia-Chun Tsai

5


e-Key based on XORs & ORs

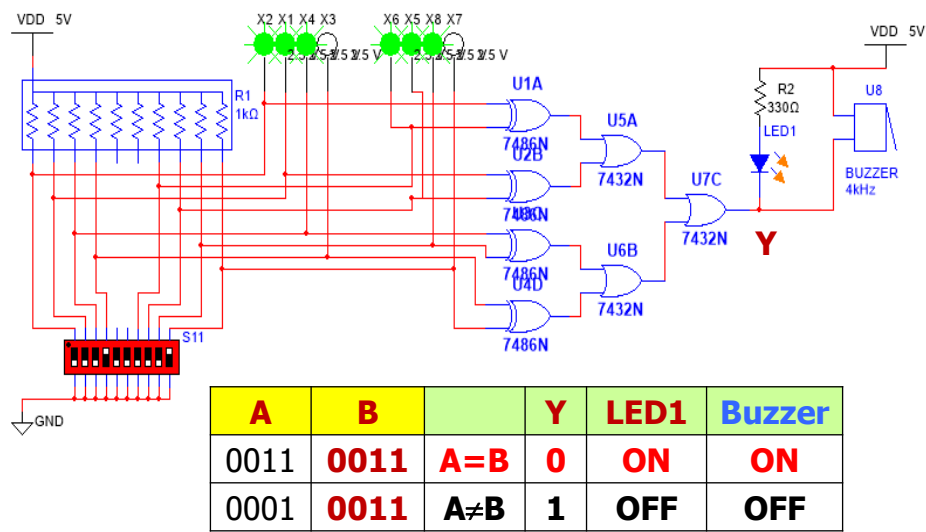

Chia-Chun Tsai

6


e-Key based on XORs & ORs

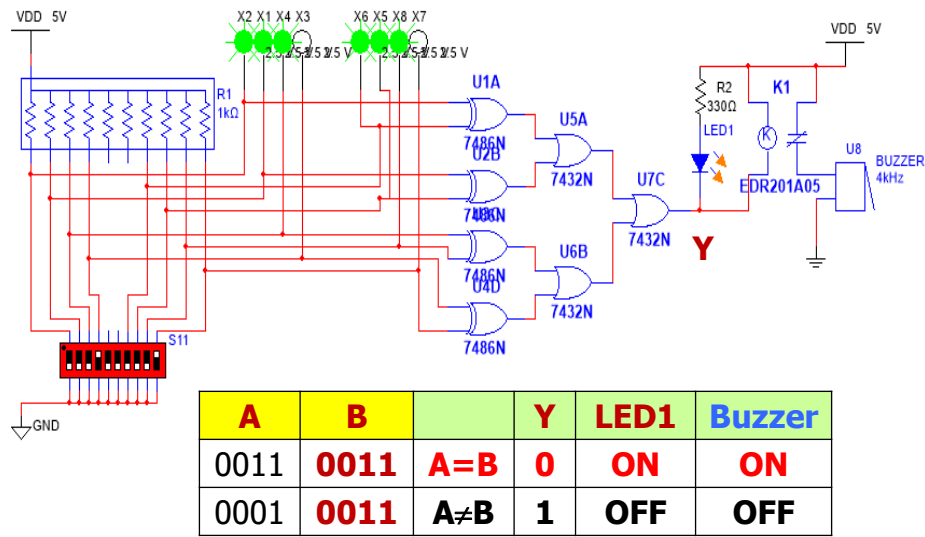

Chia-Chun Tsai


7

e-Key based on XORs & ORs

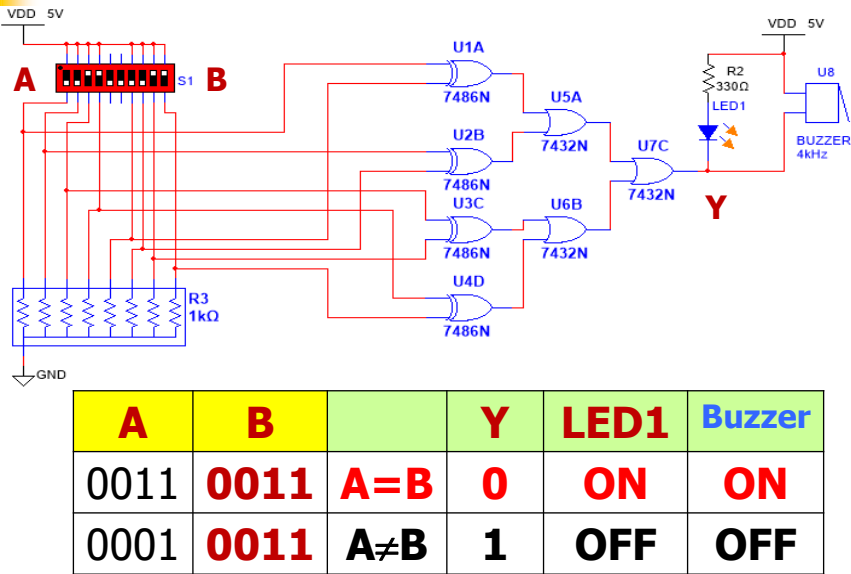


Chia-Chun Tsai

8

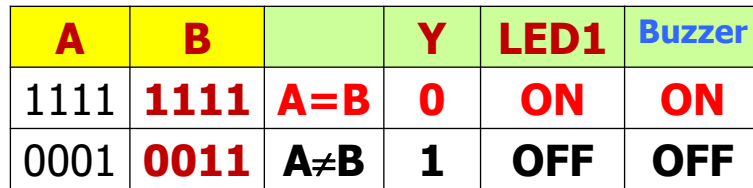


2

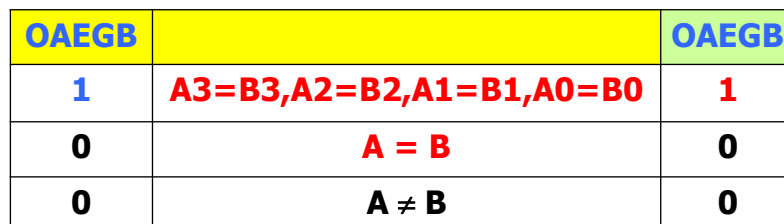

10

e-Key based on comparator 7485

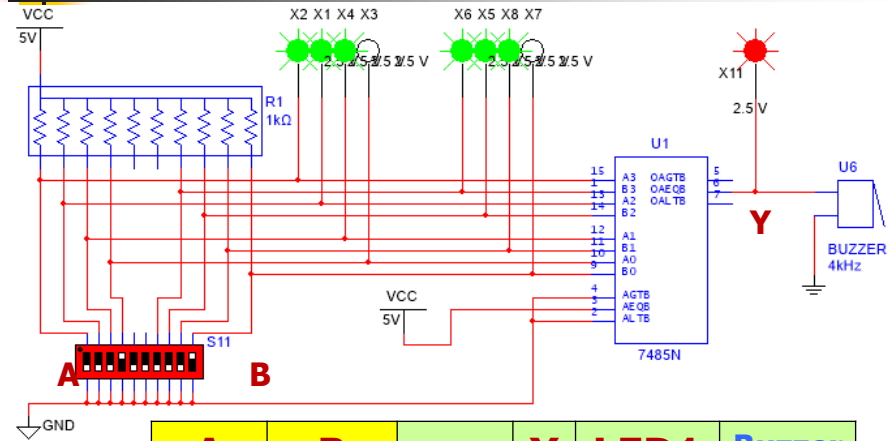


A	B		Y	LED1	Buzzer
0001	0001	A=B	1	ON	ON
0001	0011	A≠B	0	OFF	OFF

Chia-Chun Tsai

11

e-Key based on comparator 7485

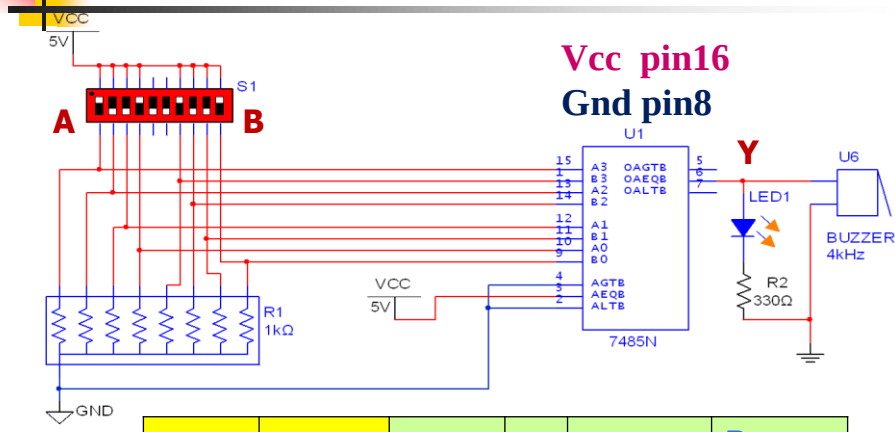


A	B		Y	LED1	Buzzer
1001	1001	A=B	1	ON	ON
0001	0011	A≠B	0	OFF	OFF

Chia-Chun Tsai

12

Eeperment-1

e-Key based on XORs & ORs

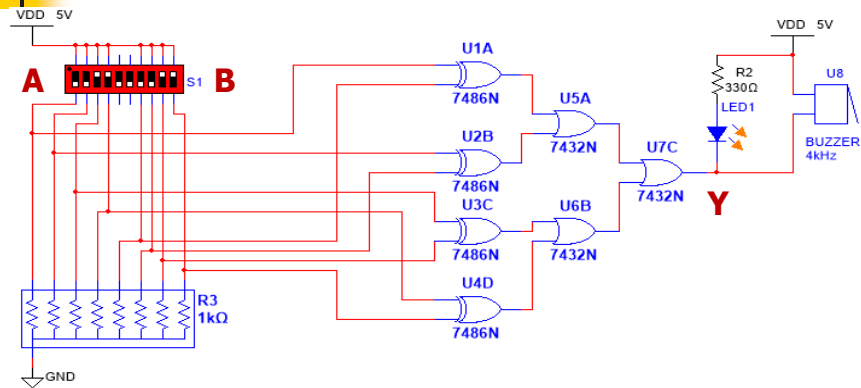


S1	Y(LED1)	Y(Buzzer)
A=B		
A≠B		

Chia-Chun Tsai

13

Experiment-2

e-Key based on comparator 7485

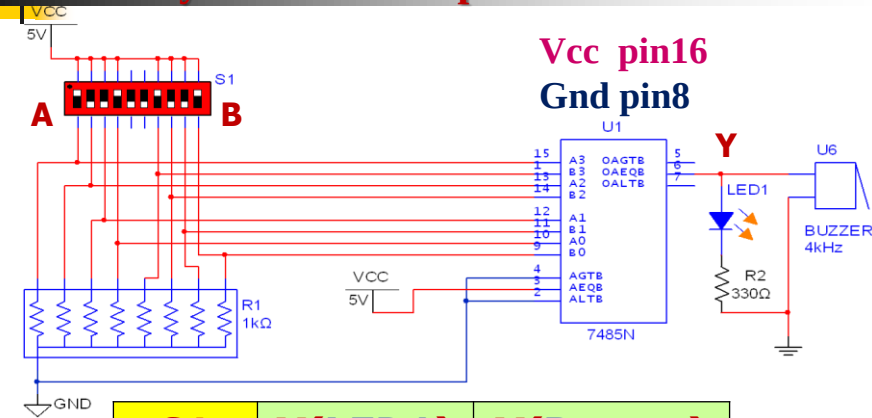

S1	Y(LED1)	Y(Buzzer)
A=B		
A≠B		

Chia-Chun Tsai

14