



Lab-11

Astable Oscillator

Chia-Chun Tsai

Objectives



- Understand the fundamental of **an oscillator**.
- Understand the fundamental of **astable multivibrator**.
- Understand the function of **a timer 555**.
- Understand various astable oscillators using **timer 555**.
- Can implement various astable oscillators using **timer 555**.


Chia-Chun Tsai

2

What is oscillator



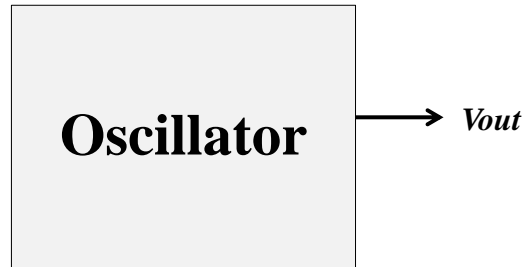- *Vout* can output a voltage waveform such as *sinusoidal*, *square*, or *triangle* waveform.





Chia-Chun Tsai

3

Astable Multivibrator



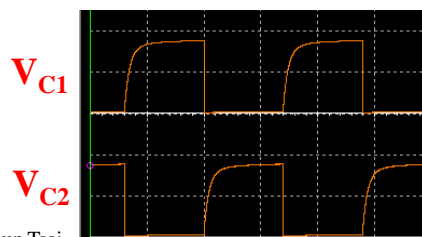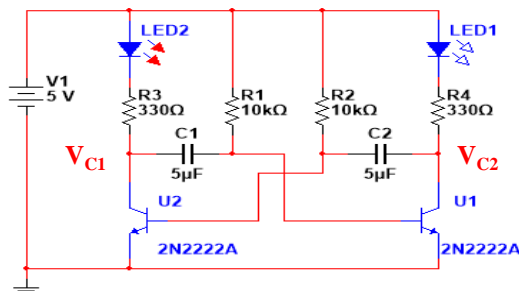- It consists of two Transistors and R/C components.



Vout: 0V~5V Square wave
 $T = 0.693(R1C1 + R2C2)$
 $T = 0.693 * 10k * 5\mu * 2 = 69.3ms$
 $F = 1/T = 1 / 69.3m$
 $= 14.43 \text{ Hz}$


Chia-Chun Tsai

4



Astable Multivibrator

- It consists of two NOTs.

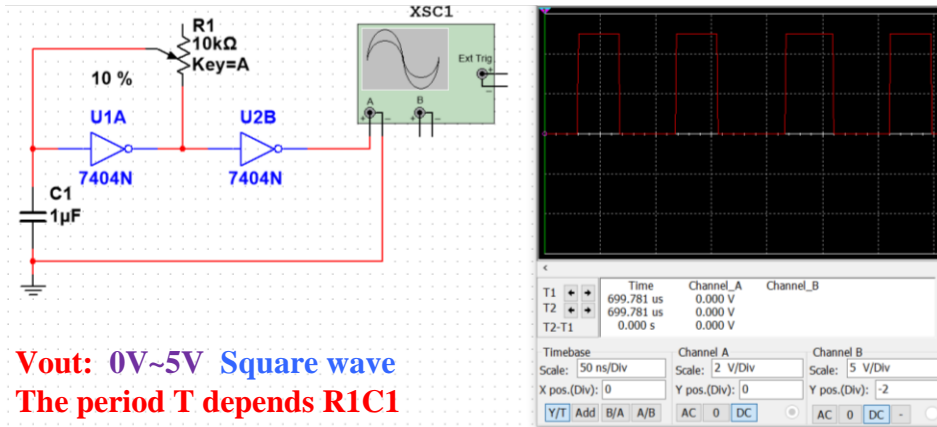


Vout: 0V~5V Square wave
The period T depends R1C1
The frequency is very high
(tens of MHz)

Chia-Chun Tsai

5



Introduction to 555 Timer

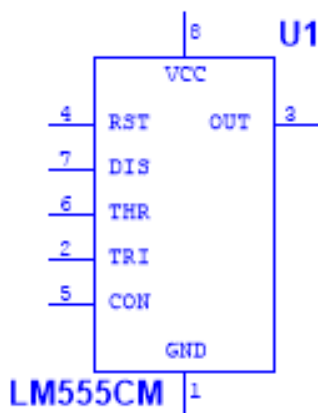

U1 Vcc(8): 5V~15V

GND(1): 0V

OUT(3): 0V or VCC

RST(Reset)(4): if RST=0V, OUT=0V

RST=Vcc if normal state

THR(Threshold)(6): if $THR \geq \frac{2}{3} V_{cc}$, then OUT=0V

DIS(Discharge)(7)): for discharging


TRI(Trigger)(2): if $TRI \leq \frac{1}{3} V_{cc}$, then OUT=Vcc

Con(Control voltage)(5): Connect 0.1μF to GND in general

Chia-Chun Tsai

6

555 Astable OSC

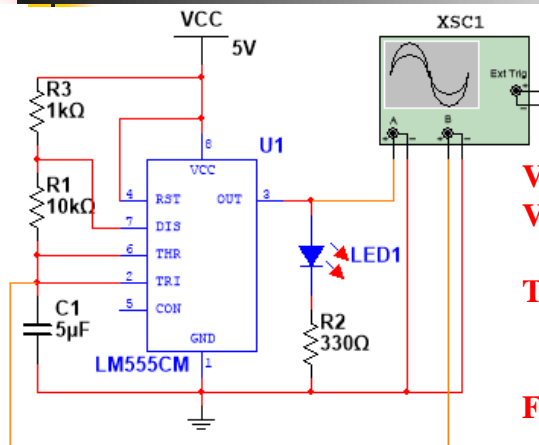

Vout: 0V~5V Square wave

Vc1: $1/3 \cdot 5V \sim 2/3 \cdot 5V$

exponential wave


$$T = 0.693 \cdot (R3 + 2R1) \cdot C1$$

$$= 0.693 \cdot (1k + 2 \cdot 10k) \cdot 5\mu$$

$$= 72.8ms$$

$$F = 1/T = 1/72.8m = 13.7Hz$$


V_{OUT}
V_{C1}

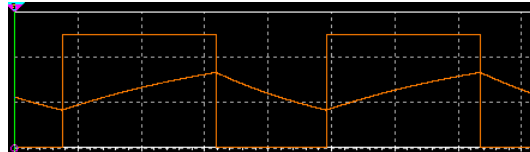

Chia-Chun Tsai

7

555 Reduced Astable OSC

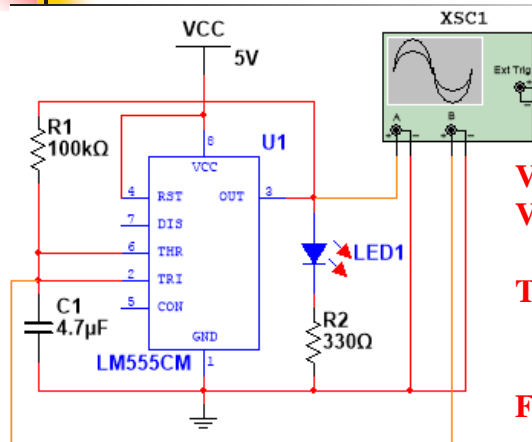

Vout: 0V~5V Square wave

Vc1: $1/3 \cdot 5V \sim 2/3 \cdot 5V$

exponential wave


$$T = 0.693 \cdot 2 \cdot R1 \cdot C1$$

$$= 0.693 \cdot 2 \cdot 100k \cdot 4.7\mu$$

$$= 651.4ms$$

$$F = 1/T = 1/651.4m \approx 1.5Hz$$

V_{OUT}
V_{C1}

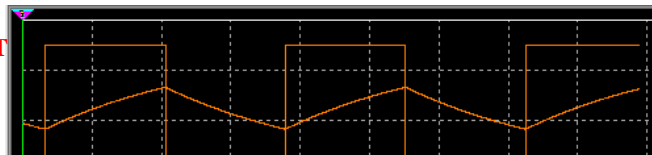


Chia-Chun Tsai

8




555 Astable

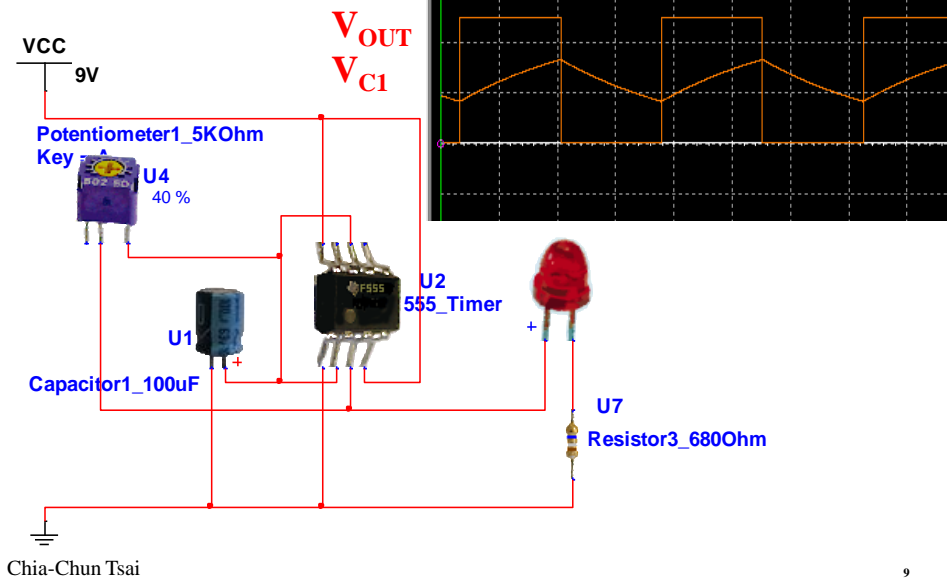

9




555 Astable Applications

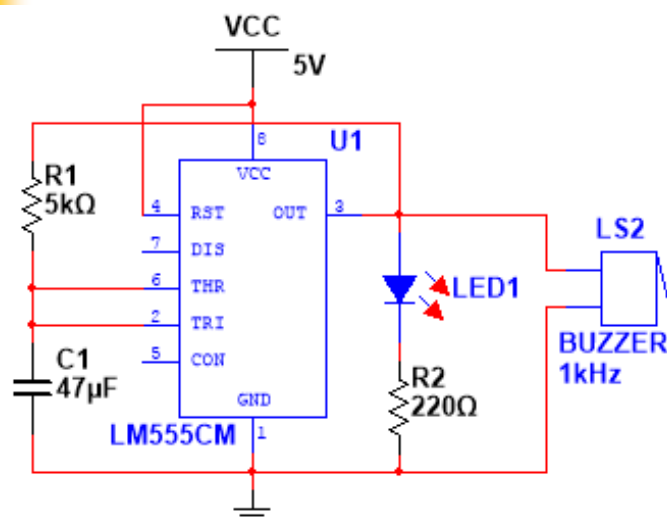

Chia-Chun Tsai

10


555 Astable Applications

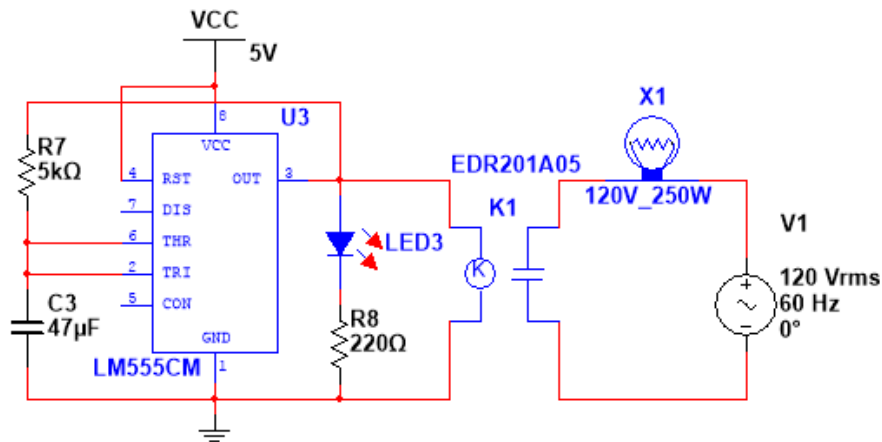

Chia-Chun Tsai

11

Dual Sound based on two 555 Astables

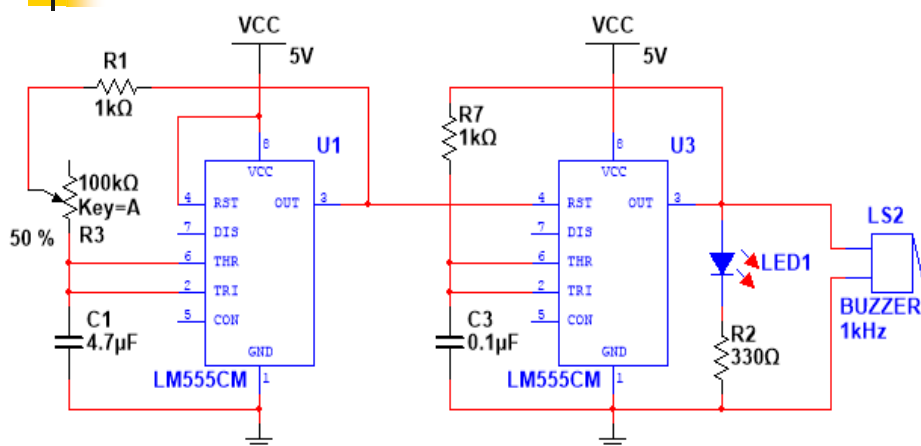


Low frequency + High frequency

LED1 or buzzer will be dual-various
by adjusting the potentiometer 100KΩ

Chia-Chun Tsai

12


Dual Sound based on two 555 Astables

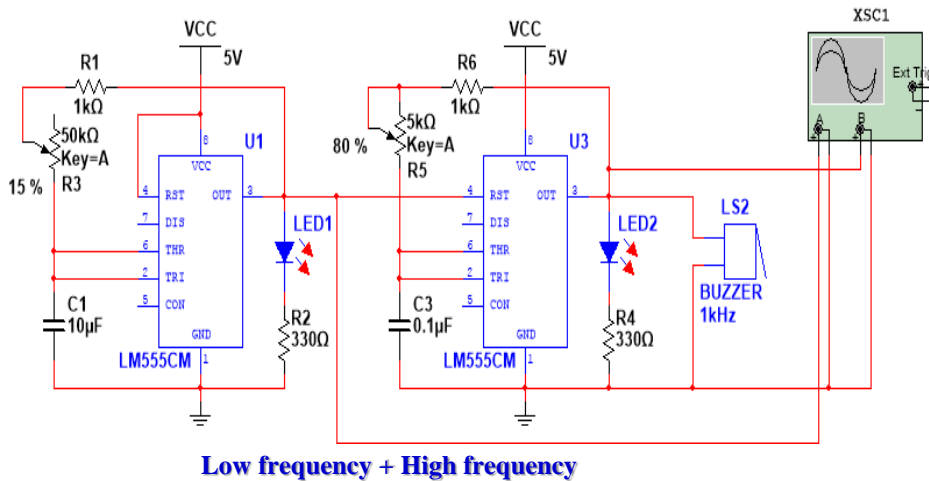

Chia-Chun Tsai

13

Experiment-1 555 Astable OSC

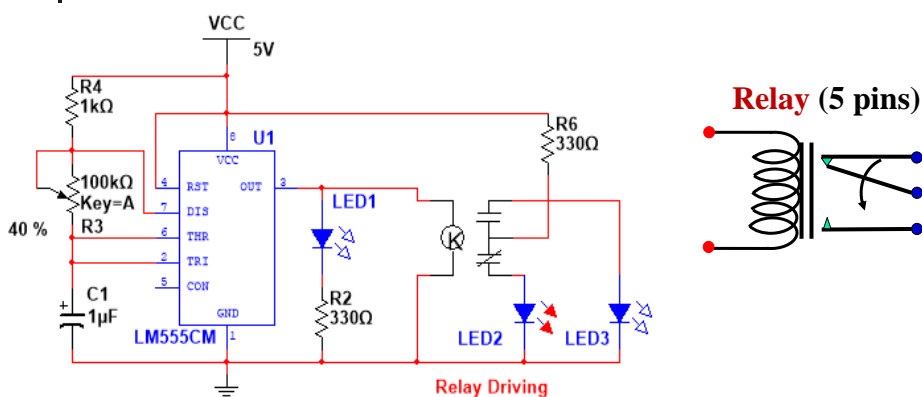


1. How about working are for **LEDs** and **Relay**?
2. What will happen for **LEDs** if **adjusting the potentiometer R3**?
3. If **LED1** can **ON/OFF** alternatively, please compute the **frequency**.

Chia-Chun Tsai

14

Experiment-1a 555 Astable OSC

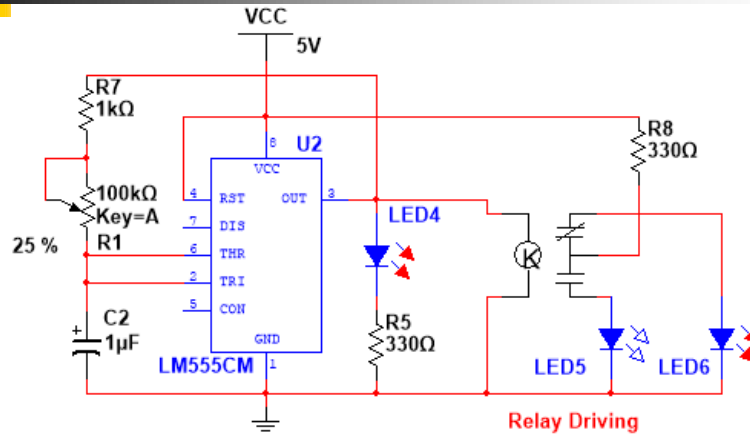


1. How about working are for **LEDs** and **Relay**?
2. What will happen for **LEDs** if adjusting the potentiometer **R3**?
3. If **LED4** can **ON/OFF** alternatively, please compute the **frequency**.

Chia-Chun Tsai

15

Experiment-2 555 Astable OSC

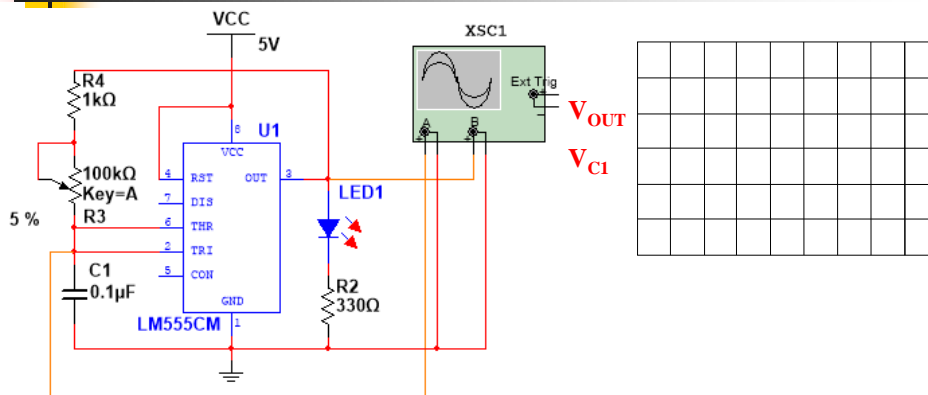


If **LED1** can **ON/OFF** alternatively by adjusting the potentiometer **R3**, then measure

Vout: _____ wave, _____ V ~ _____ V
Vc1 : _____ wave, _____ V ~ _____ V
T = _____ s and **F = 1/T =** _____ Hz

Chia-Chun Tsai

16

Experiment-2a 555 Astable OSC

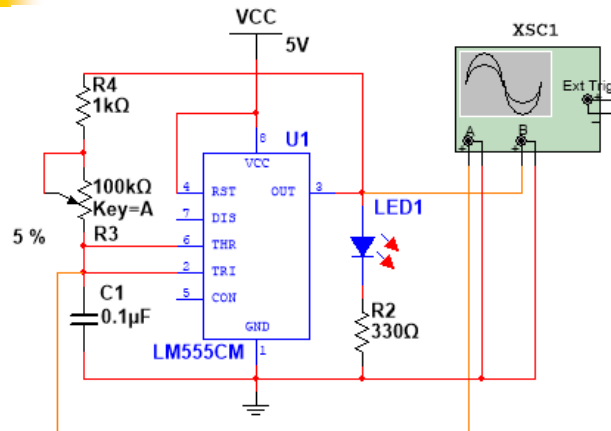

If we want a **1kHz** clock signal (i.e., **V_{out}** is square waveform with **0~5V**), how about are for the values of resistors (**R₃+R₄**) and capacitor **C₁** °