



Lab-12

555 One-Shot Latch and Flip-Flop

Chia-Chun Tsai

Objectives



- Understand the fundamental of a **one shot** based on **timer 555**.
- Understand the fundamental of an **R-S latch**.
- Understand the fundamental of **D Flip-Flop**, such as **TTL 7474**.
- Understand the fundamental of **J-K Flip-Flop**, such as **TTL 7476**.
- Understand the fundamental of **T Flip-Flop**, which is the function divided by 2.
- Can implement various combinations of **Latches and Flip-Flops**.

Chia-Chun Tsai

2



What is One-Shot

- V_{out} output a voltage for a time T , if a signal is triggered once to the input.





Chia-Chun Tsai

3



One-Shot based on 555

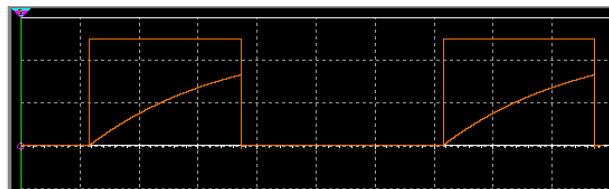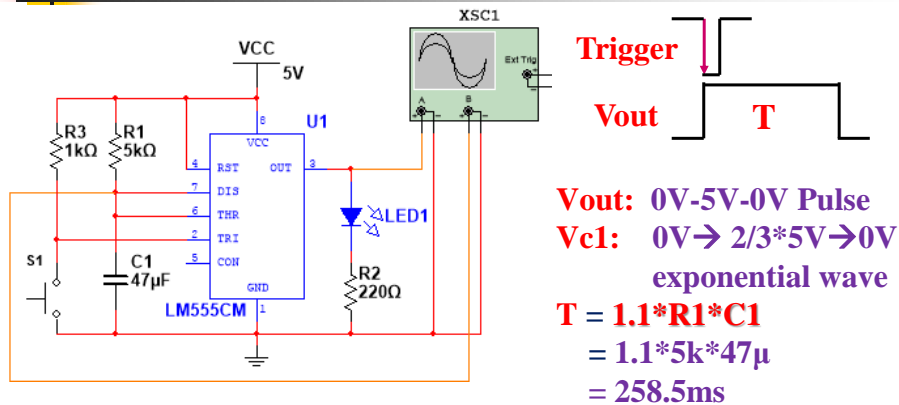


Chia-Chun Tsai

4



R-S Latch

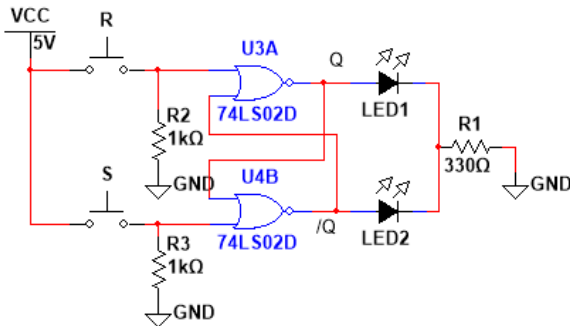- **Reset** and **Set** are active at logic High (1).
- **Set** is to Q to be 1; **Reset** is to Q to be 0.
- **Reset** and **Set** cannot be 1 at the same time.



Input		Output	
R	S	Q	/Q
0	0	hold	hold
0	1	1	0
1	0	0	1
1	1	X	X


Chia-Chun Tsai

5



/R-/S Latch

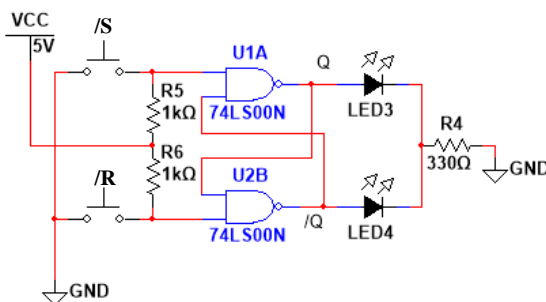- **Reset** and **Set** are active at logic Low (0).
- **/Set** is to Q to be 1; **/Reset** is to Q to be 0.
- **/Reset** and **/Set** cannot be 0 at the same time.



Input		Output	
/R	/S	Q	/Q
0	0	X	X
0	1	0	1
1	0	1	0
1	1	hold	hold


Chia-Chun Tsai

6



D Flip-Flop

TTL 7474 : Dual D Flip-Flop

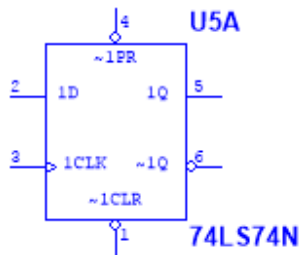

/PR	/CR	D	CK	Q
0	0	X	X	Unknow
0	1	X	X	1
1	0	X	X	0
1	1	X	X	Hold
1	1	0	0→1	0
1	1	1	0→1	1


Chia-Chun Tsai

7



J-K Flip-Flop

TTL 7476 : Dual J-K Flip-Flop

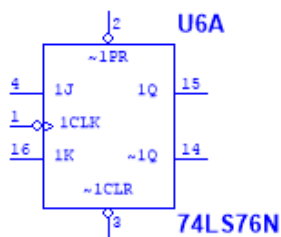


/PR	/CR	J	K	CK	Q
0	0	X	X	X	Unknow
0	1	X	X	X	1
1	0	X	X	X	0
1	1	X	X	X	Hold
1	1	0	0	0→1→0	Hold
1	1	0	1	0→1→0	0
1	1	1	0	0→1→0	1
1	1	1	1	0→1→0	Toggle

Chia-Chun Tsai

8

T Flip-Flop

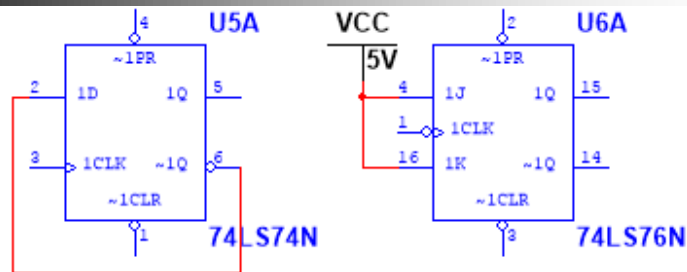

/PR	/CR	CK	Q
0	0	X	Unknown
0	1	X	1
1	0	X	0
1	1	X	Hold
1	1	0→1 or 0→1→0	Toggle


Chia-Chun Tsai

9

÷ 2 based on T Flip-Flop




Two kinds of T-FFs

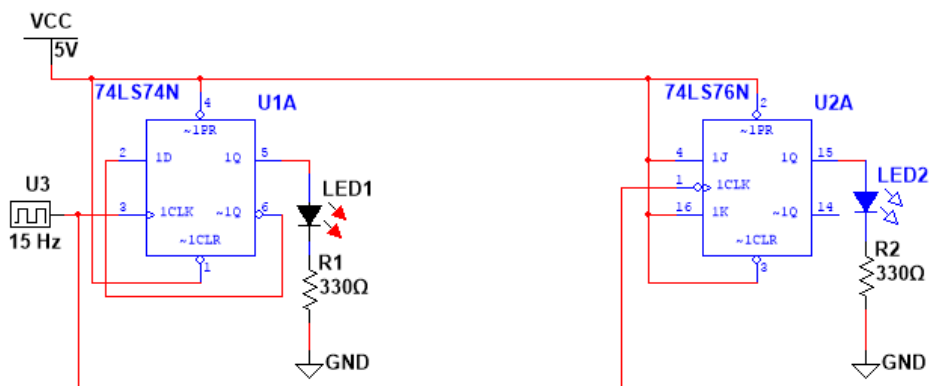

Chia-Chun Tsai

10


÷ 2 based on T Flip-Flop

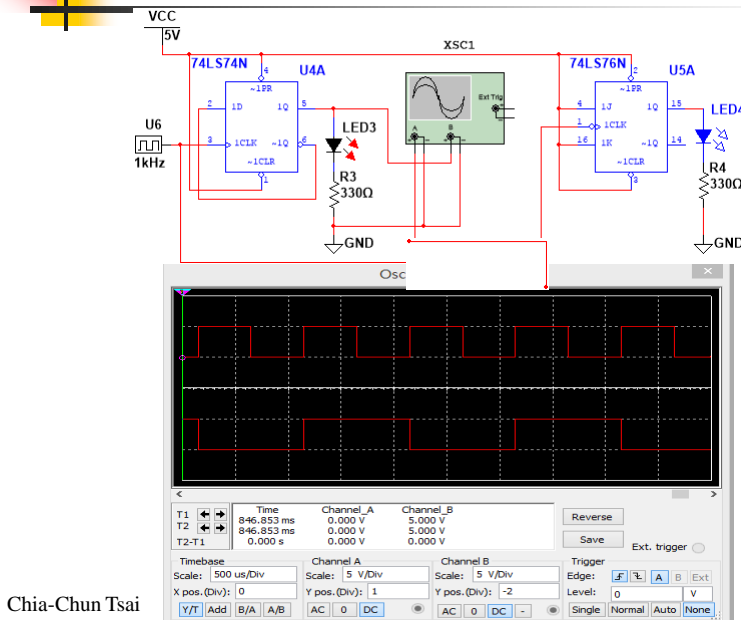

Chia-Chun Tsai

11

Experiment-1 One-Shot based on 555

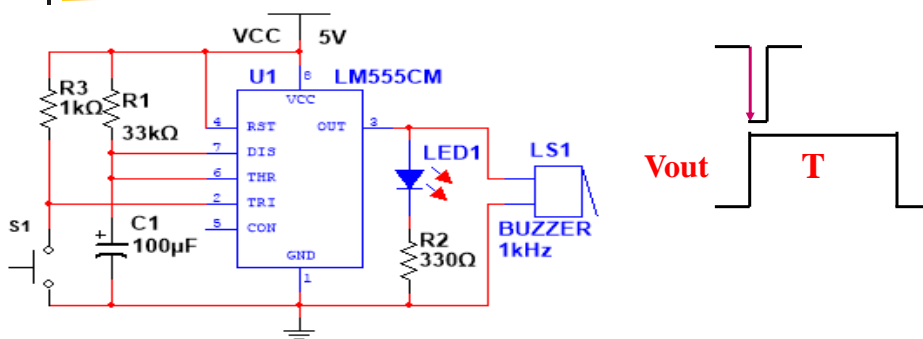


Push S1 once, LED1 & Buzzer are on for a time,
 $T = 1.1 * R1 * C1 = 1.1 * 33k * 100\mu = \underline{3.53 s}$

Chia-Chun Tsai

12

Experiment-2 /R-/S Latch

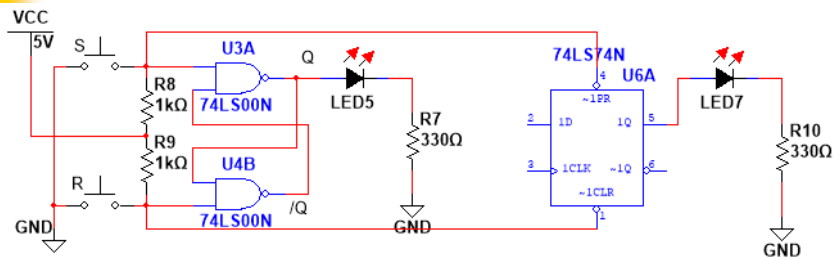

Push S once, Q is **1**
Push R once, Q is **0**

Input		Output
/R	/S	Q
1	1	Hold
1	0	1
0	1	0
0	0	X

Chia-Chun Tsai

13


Experiment-3 ÷16 based on JK FFs



Counting: 0000~1111 (÷ 16)

Push Preset once, LEDs = **1111**

Push Clear once, LEDs = **0000**

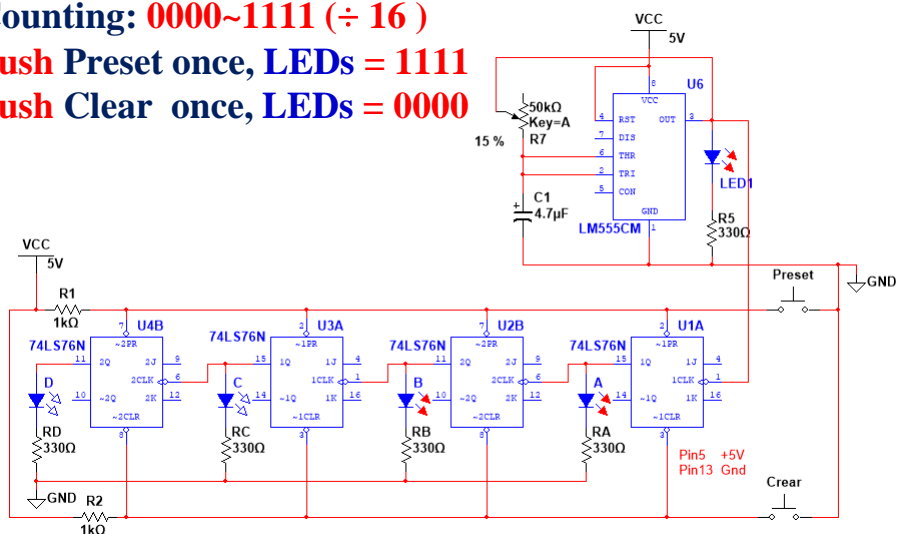

Chia-Chun Tsai

14