



# Lab-15

## One-Shot (Monostable)

Chia-Chun Tsai

### Objectives



- Understand the fundamental of **one shot** or **monostable multivibrator**.
- Understand the fundamental of a **one shot** based on **timer 555**.
- Applications based on **555 one-shot** in series.
- Understand the fundamental of a **one shot** based on **TTL 74121**.
- Applications based on **74121 one-shot** in series.

Chia-Chun Tsai

2

## What is One-Shot




- ***V<sub>out</sub>*** output a voltage for a time ***T***, if a signal is triggered once to the input.



Chia-Chun Tsai

3

## 555 Timer


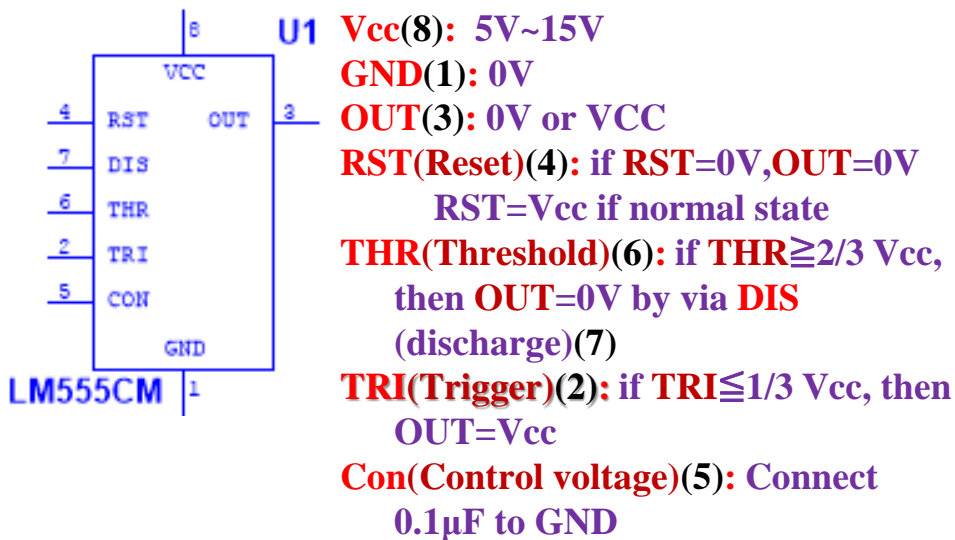


Chia-Chun Tsai

4



## One-Shot based on 555

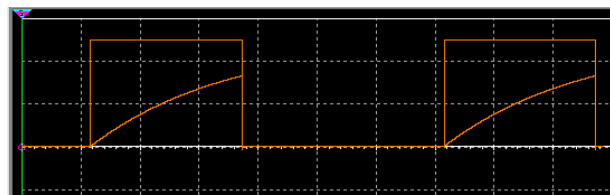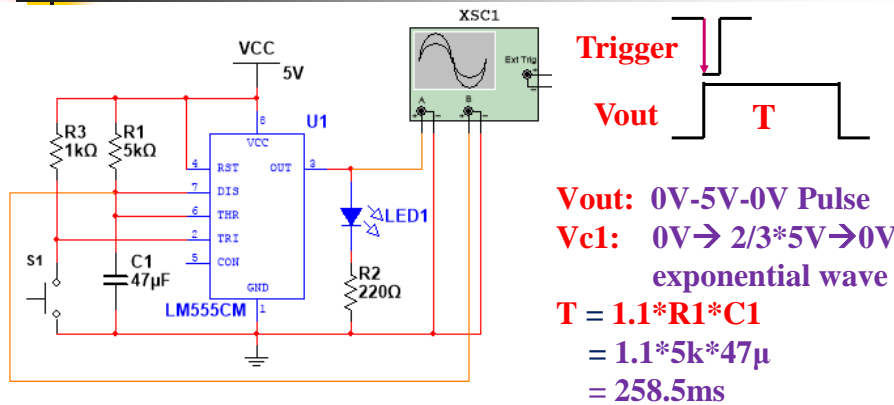


Chia-Chun Tsai

5




## 555 One-Shot Applications

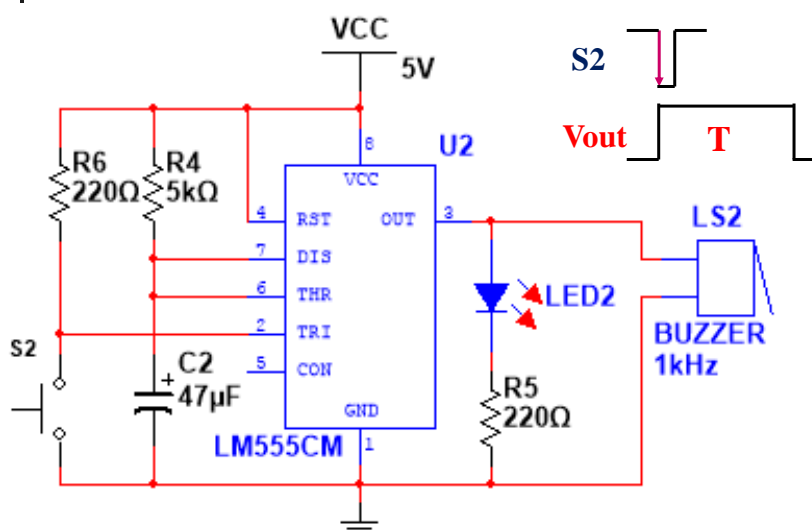

Chia-Chun Tsai

6

# One-Shot to Turn on a Lamp

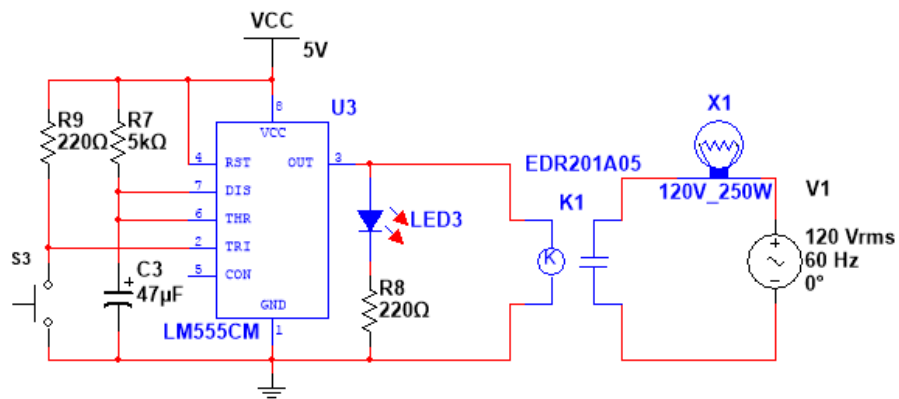


Chia-Chun Tsai

7

# Relay




## DC-6V Relay

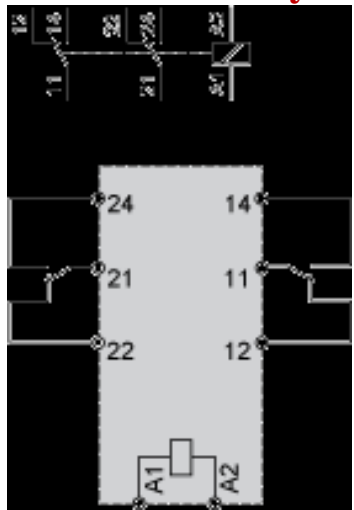

Chia-Chun Tsai


## DC-5V Relay

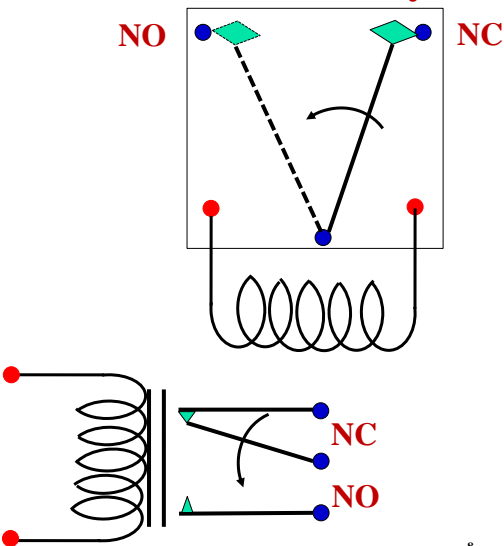

8



## 555 One-Shot in Series

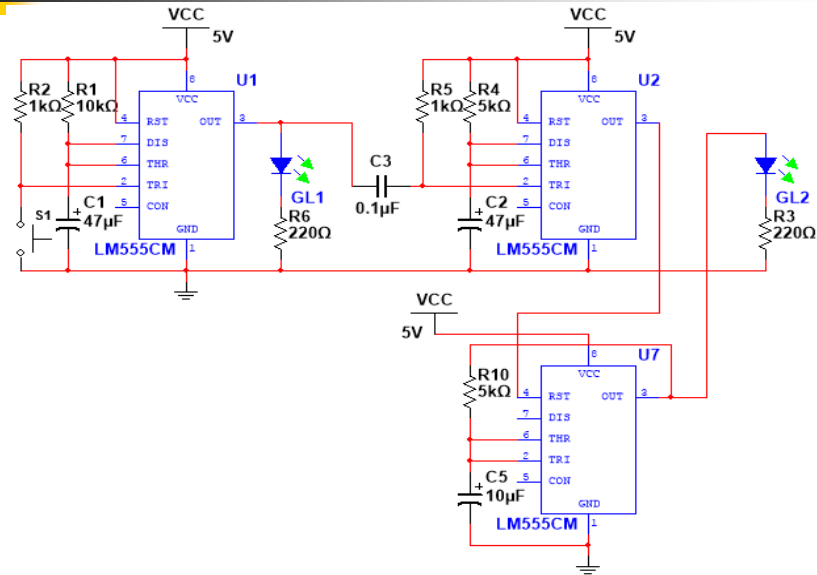


Chia-Chun Tsai

9




## Traffic Signal based on 555 One-Shot

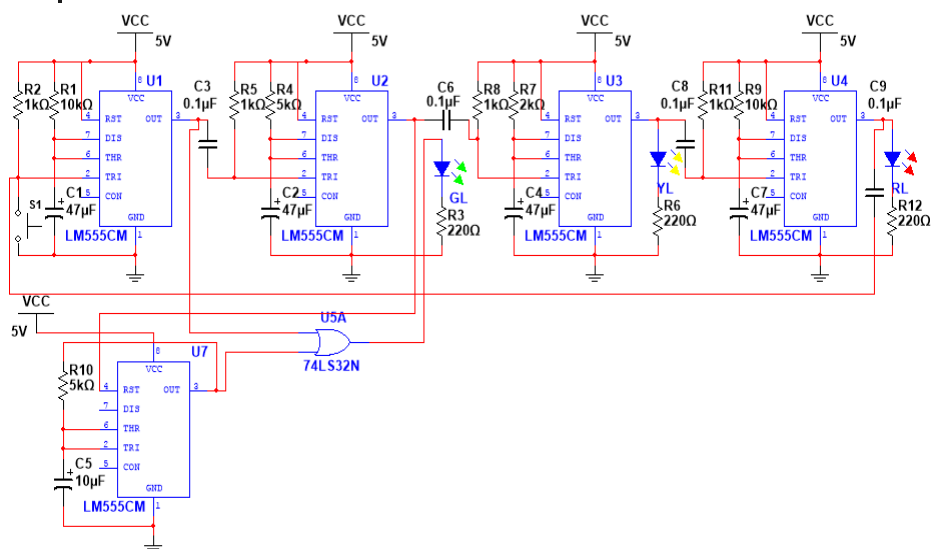

Chia-Chun Tsai

10

# One-Shot based on 74121

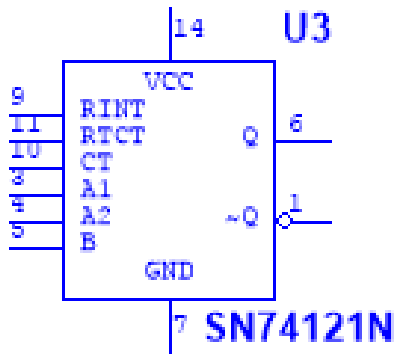


/A1	/A2	B	Q
1→0	0	X	0
1→0	X	0	0
1→0	1	1	pulse
0	1→0	X	0
X	1→0	0	0
1	1→0	1	pulse
1	1	0→1	0
0	X	0→1	pulse
X	0	0→1	pulse


Chia-Chun Tsai

11

# Two RC Choices for 74121

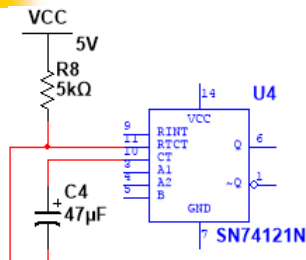

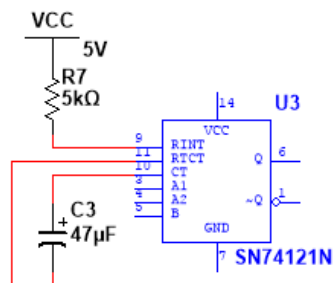**Q: 0V-5V-0V Pulse**  
 $T=0.693RC=0.693*5k*47\mu$   
 $=162.855ms$   
**R= 1.4kΩ~40kΩ**  
**C=0~1000μF**




**Q: 0V-5V-0V Pulse**  
 $T=0.693(R+2k\Omega)C$   
 $=0.693*(5k+2k)*47\mu$   
 $=227.997ms$   
**R= 1.4kΩ~40kΩ**  
**C=0~1000μF**

Chia-Chun Tsai

12

# 74121 One-Shot Applications

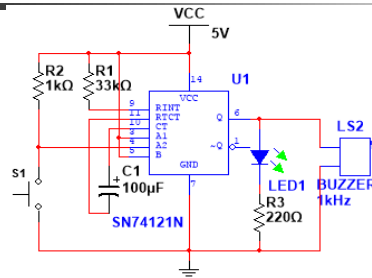

**Q: 0V-5V-0V Pulse**


**$T = 0.693(R + 2k\Omega)C$**

$$= 0.693 * (33k + 2k) * 100\mu$$

$$= 2.4255s$$

**$R = 1.4k\Omega \sim 40k\Omega$**


**$C = 0 \sim 1000\mu F$**

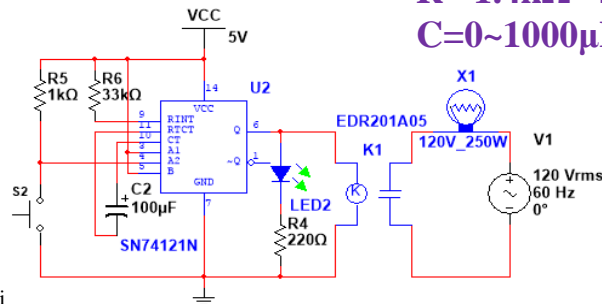

Chia-Chun Tsai

13


# 74121 One-Shot in Series

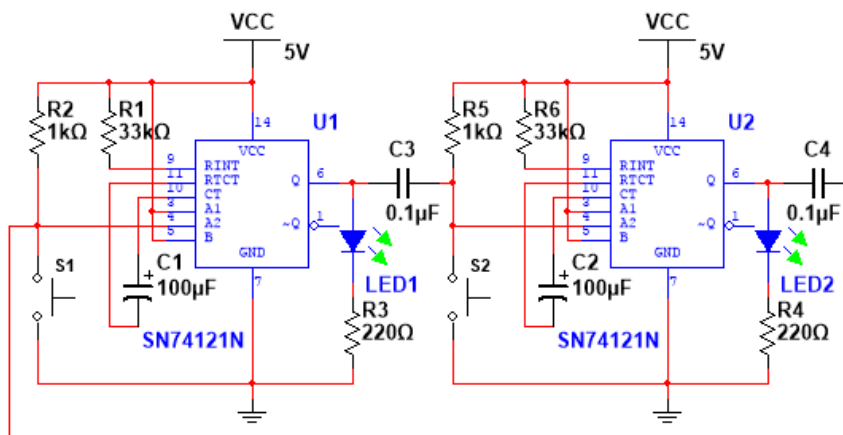

Chia-Chun Tsai

14

## Experiment-1 One-Shot based on 555

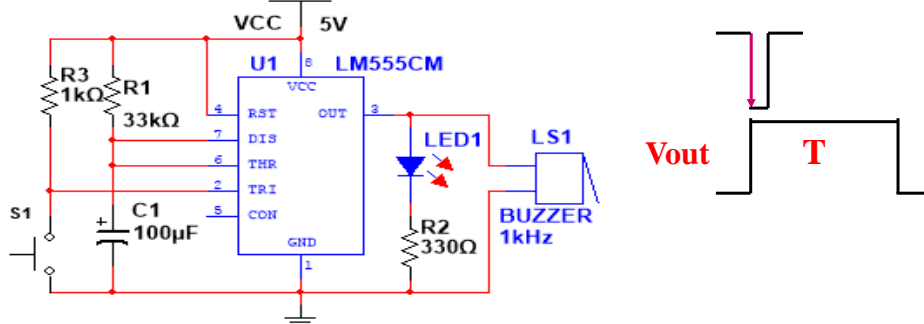

**Vout:** 0V-5V-0V Pulse


**Vc1:** 0V →  $\frac{2}{3} * 5V \rightarrow 0V$  exponential waveform

$$T = 1.1 * R1 * C1 \\ = 1.1 * 33k * 100\mu = \underline{3.53 \text{ s}}$$

Chia-Chun Tsai

15

## Experiment-2 One-Shot based on 74121

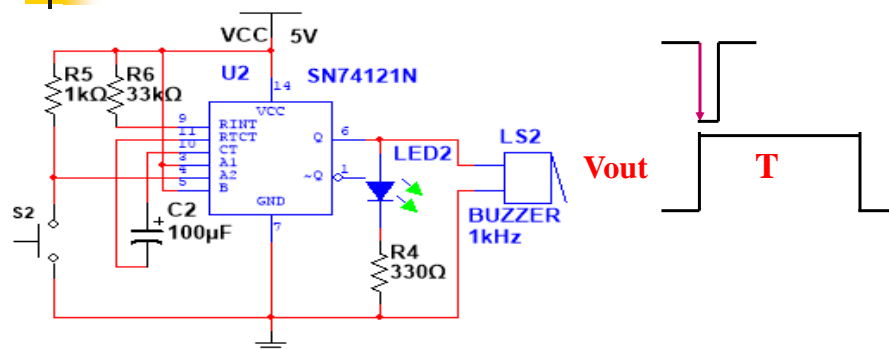

**Q:** 0V-5V-0V Pulse

$$T = 0.693(R + 2k\Omega)C = 0.693 * (33k + 2k) * 100\mu \\ = \underline{2.4255 \text{ s}}$$


Chia-Chun Tsai

16



## Experiment-3

### One-Shot Application: Roulette Game

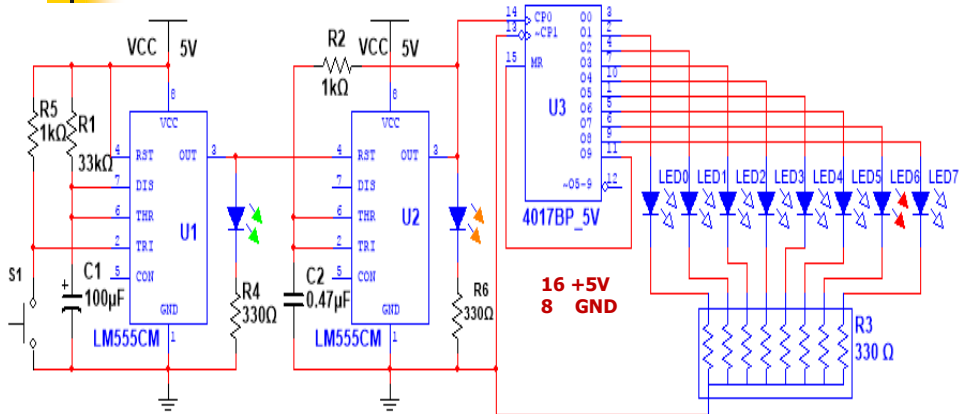

Push S1 once → One Shot  
 OUT: 0V-5V-0V Pulse  
 $T = 1.1 \cdot R1 \cdot C1$   
 $= 1.1 \cdot 33k \cdot 100\mu = 3.53 \text{ s}$

If RST=+5v → Astable OSC  
 OUT: 0-5V Square wave  
 $T = 1.4 \cdot R1 \cdot C1$   
 $= 1.4 \cdot 1k \cdot 0.47\mu = 0.658 \text{ ms}$   
 $f = 1/T = 1/0.658 = 1.5 \text{ Hz}$

If Astable OSC is work  
 → Only one LED on one time  
 from left to right

Chia-Chun Tsai

17