

ID: _____ Name: _____ Score: _____

*Note: Each problem has one point.*1. Please give briefly description in function for the following four instruments.

(a) DMM:








(b) Power Supply:

(c) Function Generator:


(d) Oscilloscope:

2. Please use DMM to check a longer wire whether was broken or not.3. In your experiments by using TTL/CMOS gates with $V_{CC}/V_{DD}=5V$, please give your measured volts for typical logic "1" and "0".


logic "1" = _____ V and logic "0" = _____ V

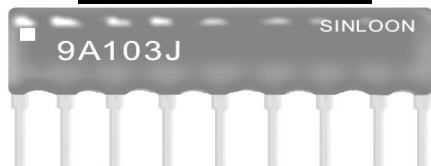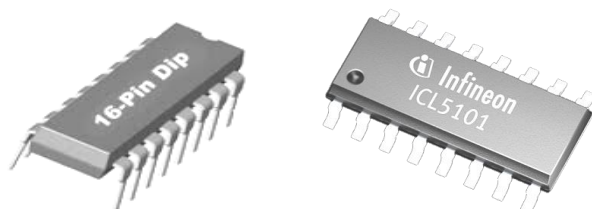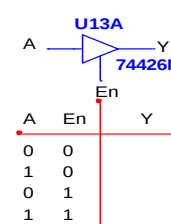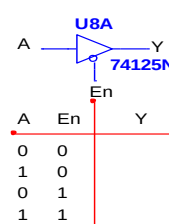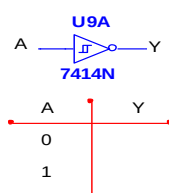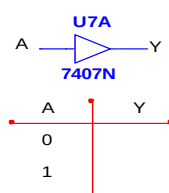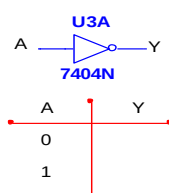4. Please mark the pin number of a packed-resistor and draw down their internal resistor network.5. Please use DMM to check a LED whether is OK or damaged.6. Please mark the pin number and their Vcc and Gnd for the following two typical ICs.7. Please fill the following truth tables for each logic gate.

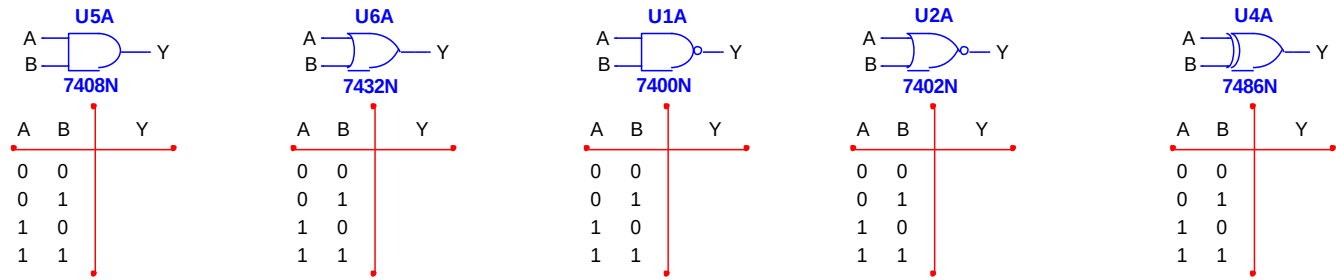8. Please fill the following **truth tables for each logic gate.**




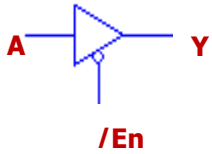9. Please fill the following **truth tables for each logic circuit.**




/En	A	Y
0	0	
0	1	
0		
1	0	

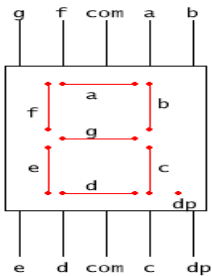
10. Please use **DMM** to **recognize the 7-segment display whether is CA** (common anode) or **CK** (common cathode).




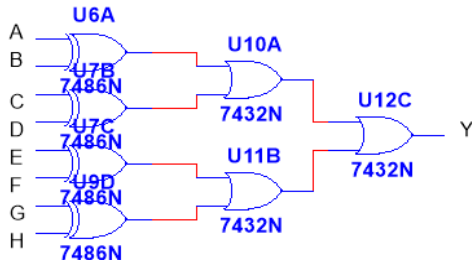
11. Please show the respective **output Y** to the inputs of (a) **ABCDEFGH = 00001111** and (b) **ABCDEFGH = 11001100**.




12. Draw the **equivalent logic gate.**

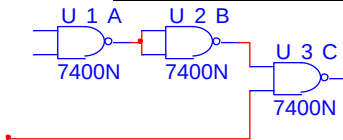

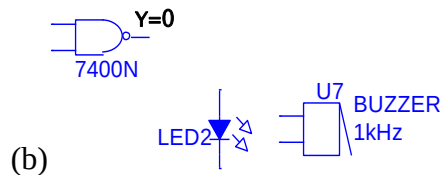
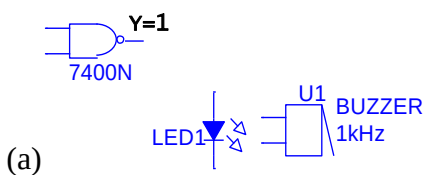
13. (a) Please connect the high-active driving such that both LED and Buzzer are on if **Y=1**.
 (b) Please connect the low-active driving such that both LED and Buzzer are on if **Y=0**.



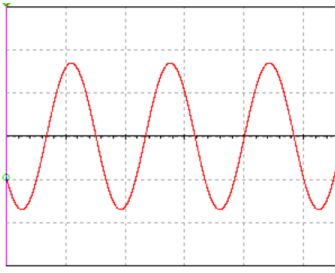14. Please determine **the voltage amplitude and frequency** of a sinusoidal waveform on a scope with the **voltage scale 2V/div** and **time scale 2ms/div**.



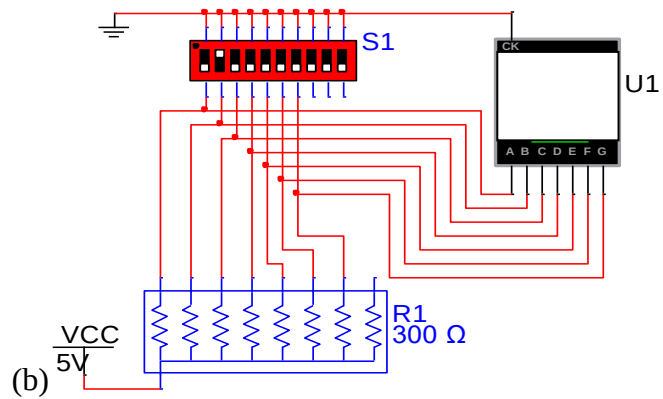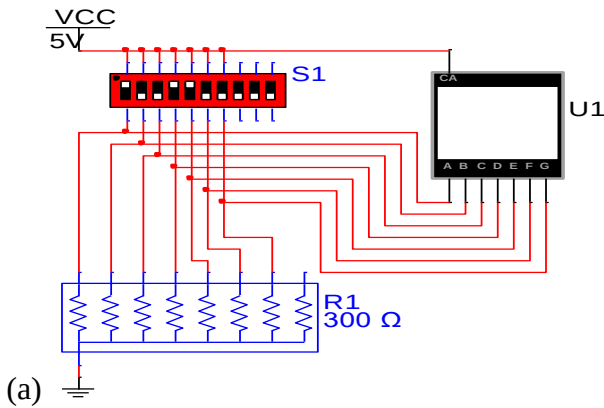15. Please **show the respective displayed number** for the following circuits (a) and (b).



16. Given a **4-bit e-key** as below, please **explain that LED1, LED2, and Buzzer are how to work** under the various conditions of comparing two 4-bits A and B.

